

# **Revisit: Passive elements & Filters**

## Impedance:

Passive elements' - Resistive, inductive & capacitive

## Ohm's law:

The voltage across a conducting material is directly proportional to the current flowing through the material.

$$V = IZ$$

# Resistor





$$V = IR$$


$$R = \frac{V}{I} \rightarrow \textit{resistance}$$

$$G = 1/R \rightarrow \textit{conductance}$$


$$R = R_1 + R_2 \quad \text{In series}$$
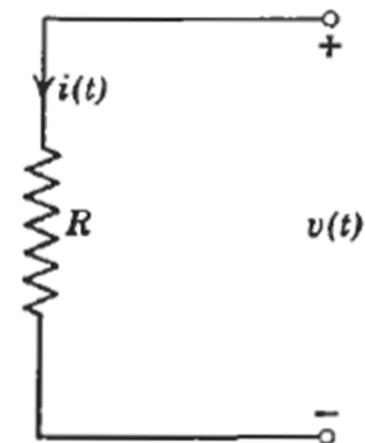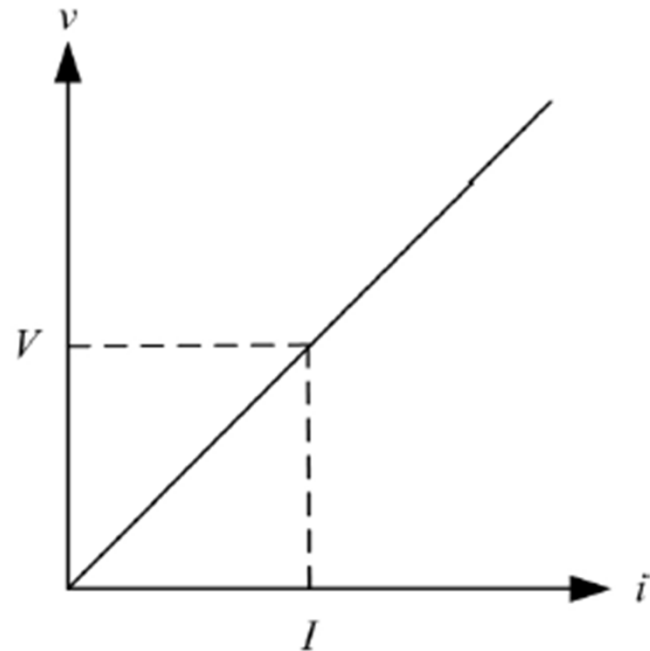
$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \quad \text{In parallel}$$



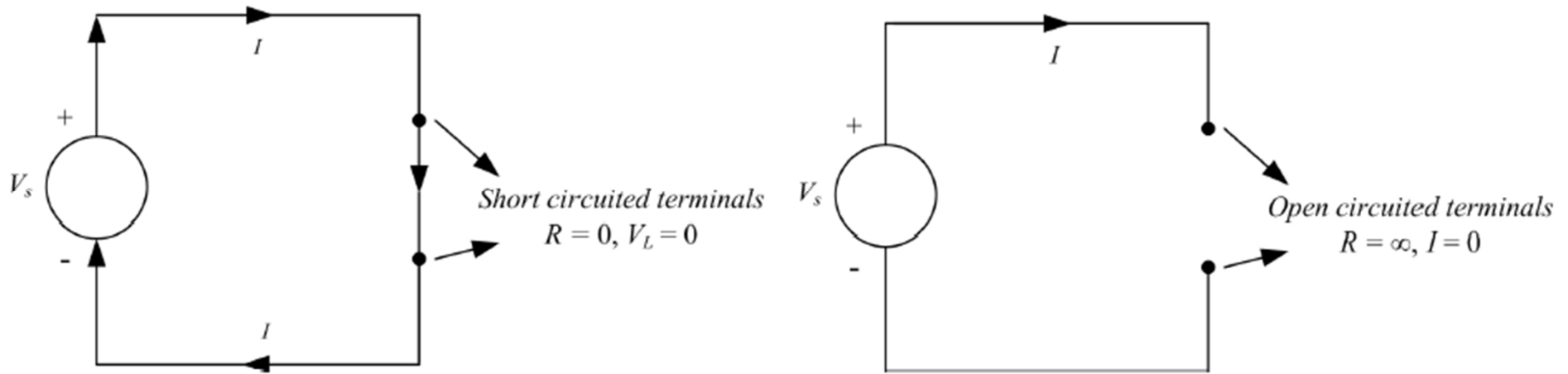

## Voltage source: Direct & Alternating

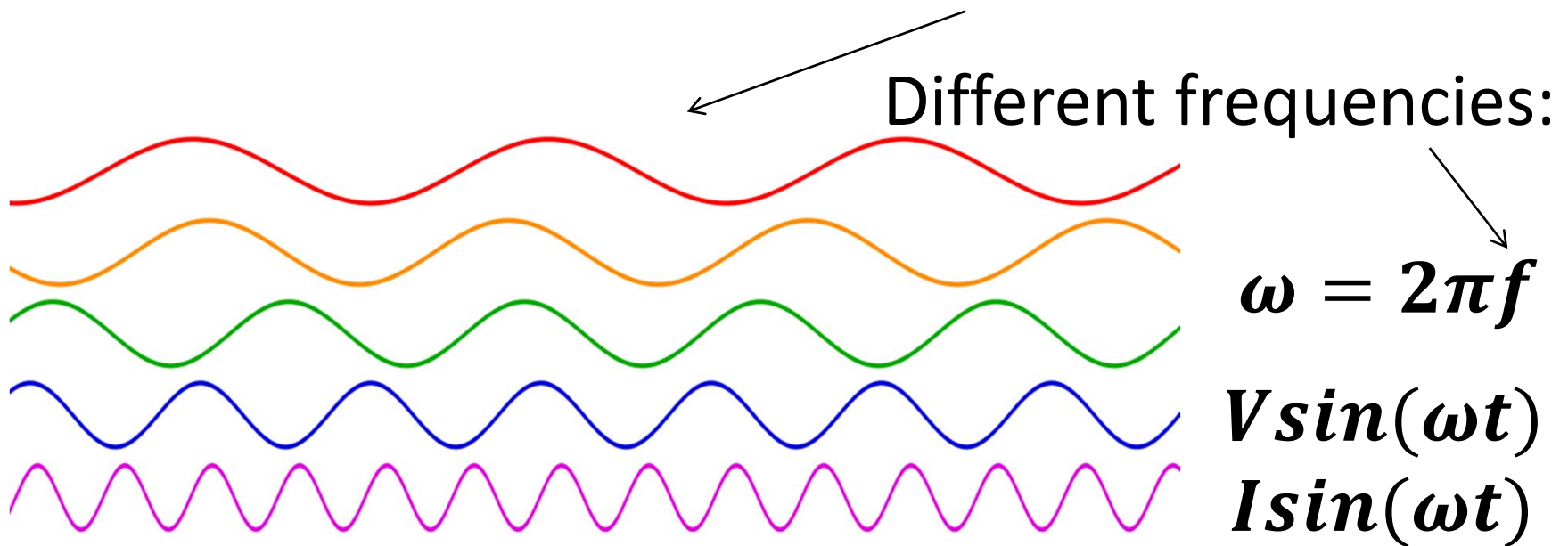

## Capacitor


$$I = C \frac{dV}{dt}, C \rightarrow \text{capacitance}$$

$$V = I \frac{1}{j\omega C}$$

$$\text{Impedance: } \frac{1}{j\omega C}, \text{ capacitive reactance} \rightarrow X_C = \frac{1}{\omega C}$$

Magnitude
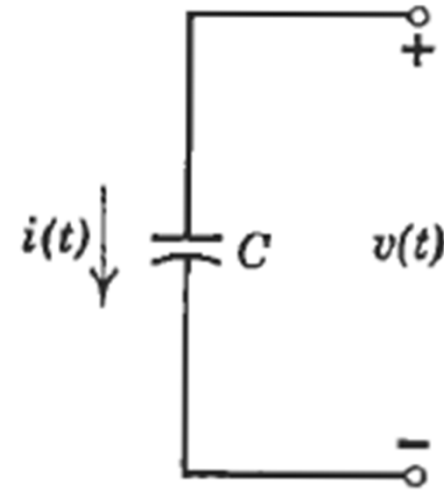
$$X_C \rightarrow \infty \text{ as } \omega \rightarrow 0 \text{ (DC)}$$




Capacitor is a open circuit for DC alone!

## Inductor

$$V = L \frac{dI}{dt}, L \rightarrow \text{inductance}$$

$$V = j\omega LI$$

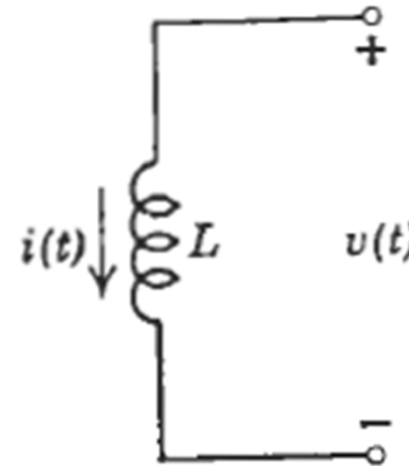

*Impedance:  $j\omega L$ , inductive reactance  $\rightarrow X_L = \omega L$*

Magnitude


$$X_L \rightarrow 0 \text{ as } \omega \rightarrow 0 \text{ (DC)}$$

Inductor is a short circuit for DC alone!

## Kirchoff's Laws:

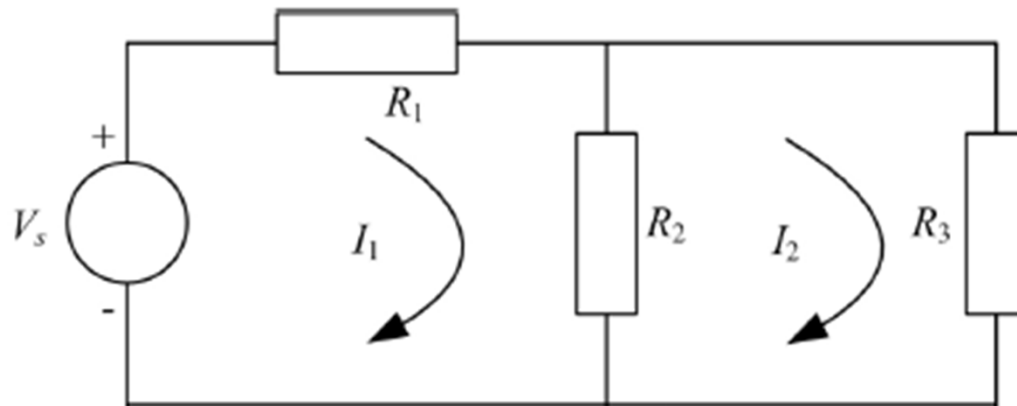
### Voltage law:

The sum of all the voltages (rises and drops) around a closed loop is equal to zero.



$$V_s = I_1 R_1 + (I_1 - I_2) R_2$$

$$0 = I_2 R_3 - (I_1 - I_2) R_2$$

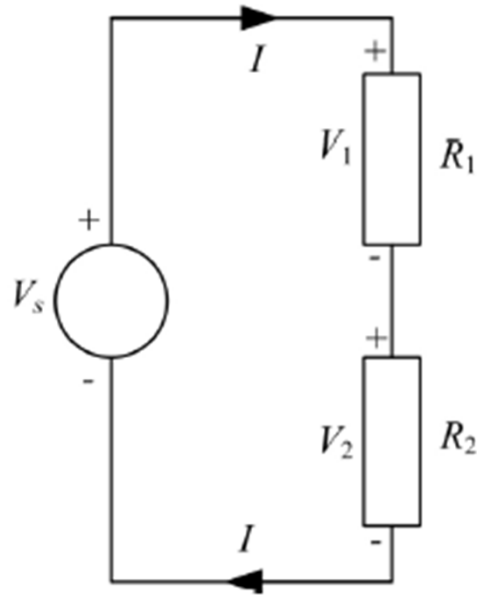

$$KVL: V_s = V_1 + V_2$$


Voltage divider rule

$$V_1 = \frac{R_1}{R_1 + R_2} V_s, V_2 = \frac{R_2}{R_1 + R_2} V_s$$



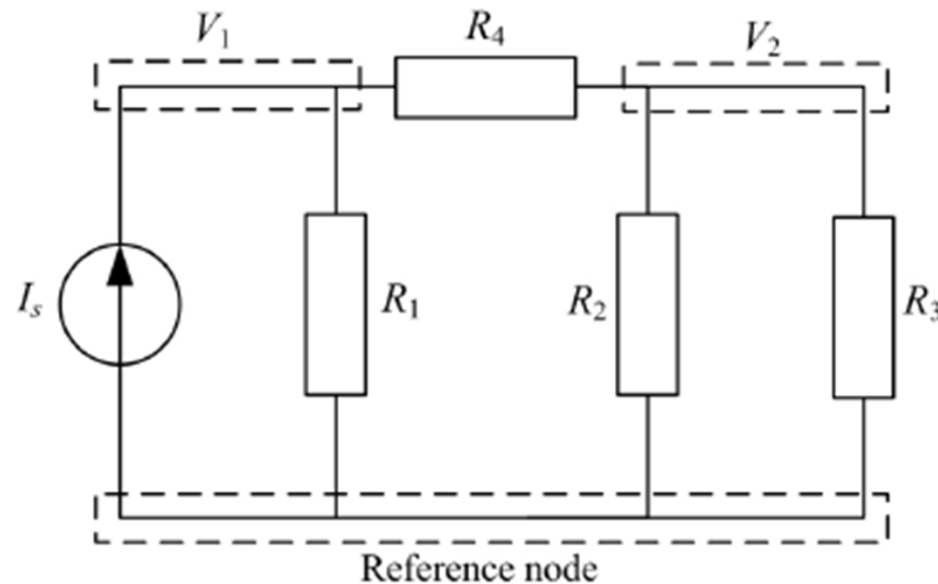
## Current law:

The algebraic sum of all the currents entering or leaving a node in an electric circuit is equal to zero


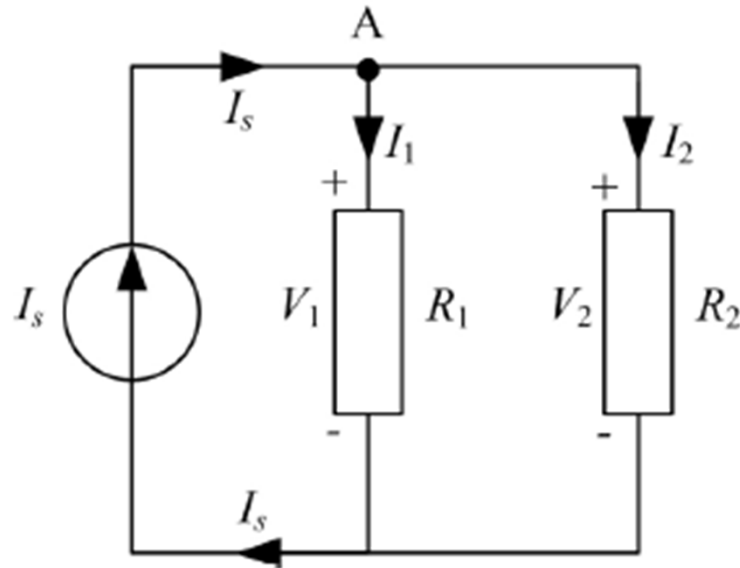
$$I_s = V_1/R_1 + (V_1 - V_2)/R_4 \qquad 0 = -\frac{V_1 - V_2}{R_4} + \frac{V_2}{R_2} + \frac{V_2}{R_3}$$





**KCL:**  $I_s = V_1/R_1 + V_2/R_2$

Current divider rule


$$I_1 = \frac{R_2}{R_1 + R_2} I_s, I_2 = \frac{R_1}{R_1 + R_2} I_s$$
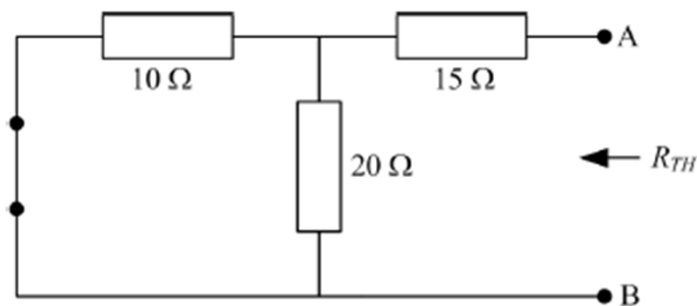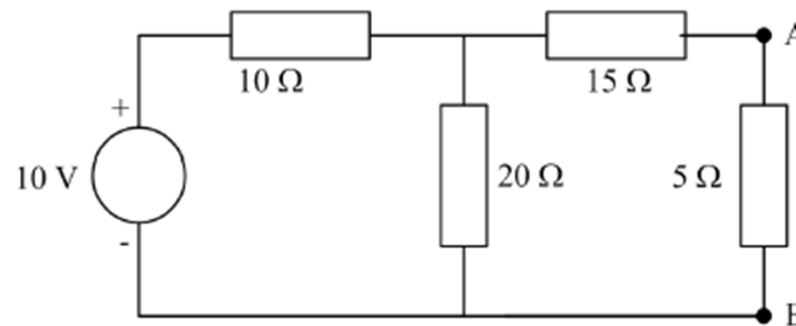
## Thevenin's Theorem:

Any two-terminal linear circuit of resistor and sources can be replaced by an equivalent circuit with a single voltage source in series with a resistor.



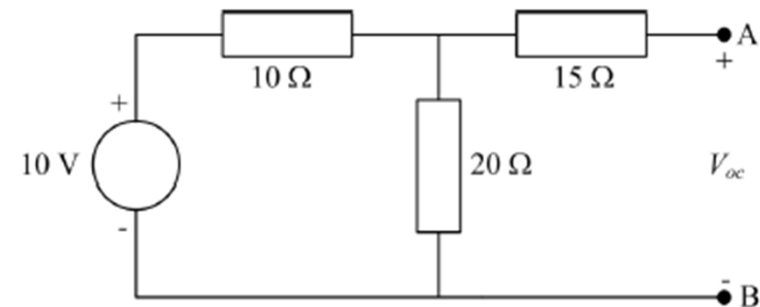
$$R_{TH} = (10 \parallel 20) + 15 = \frac{10 \times 20}{10 + 20} + 15 = 21.67 \, \Omega$$




$$V_{TH} = V_{oc} = 10 \frac{20}{10 + 20} = 6.67 \, \text{V}$$
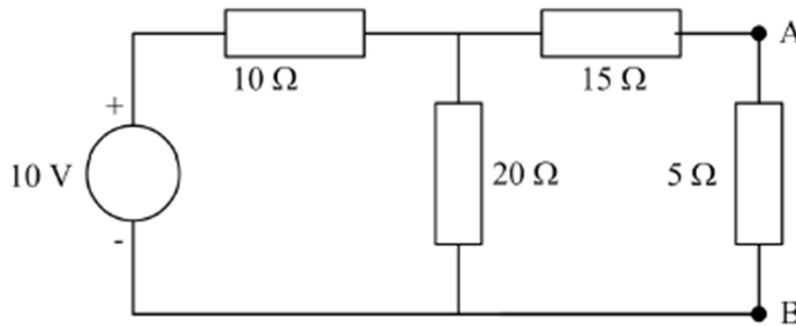
## Norton's Theorem:

Any two-terminal linear circuit of resistor and sources can be replaced by an equivalent circuit with a single current source in parallel with a resistor.





$$R_N = 21.67 \Omega$$

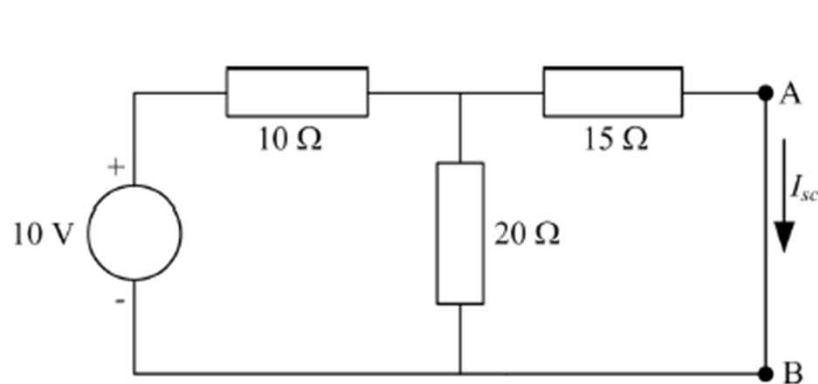


$$R_{eq} = (15 || 20) + 10 = \frac{15 \times 20}{15 + 20} + 10 = 18.57 \Omega$$

$$I_s = \frac{V_s}{R_{eq}} = \frac{10}{18.57} = 0.54 \text{ A}$$
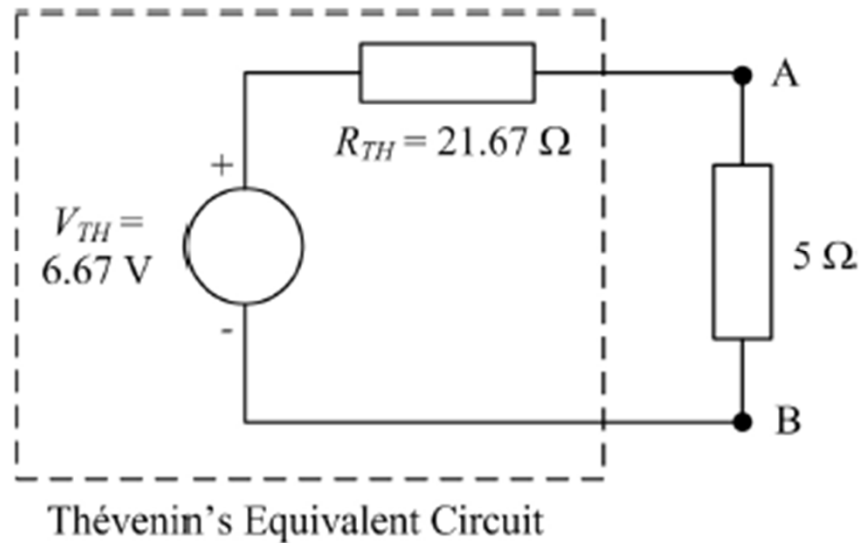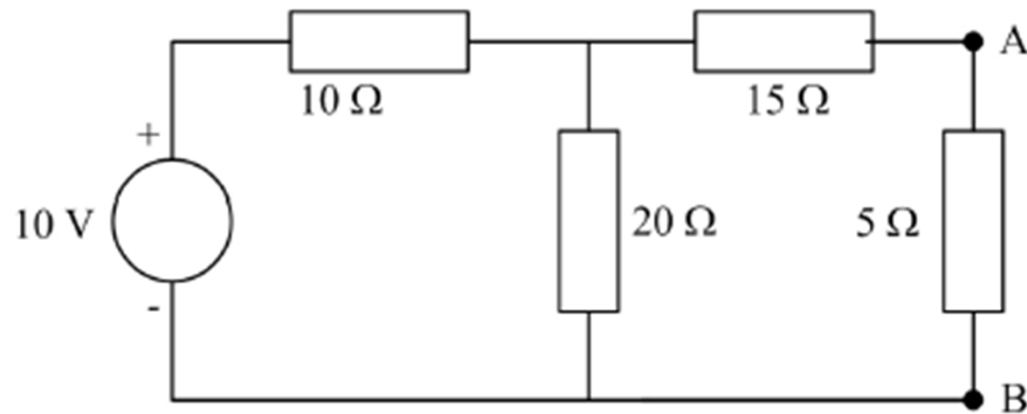
$$I_N = I_{sc} = I_s \frac{20}{15 + 20} = 0.54 \frac{20}{35} = 0.31 \text{ A}$$



$$V_{TH} = I_N R_{TH}$$

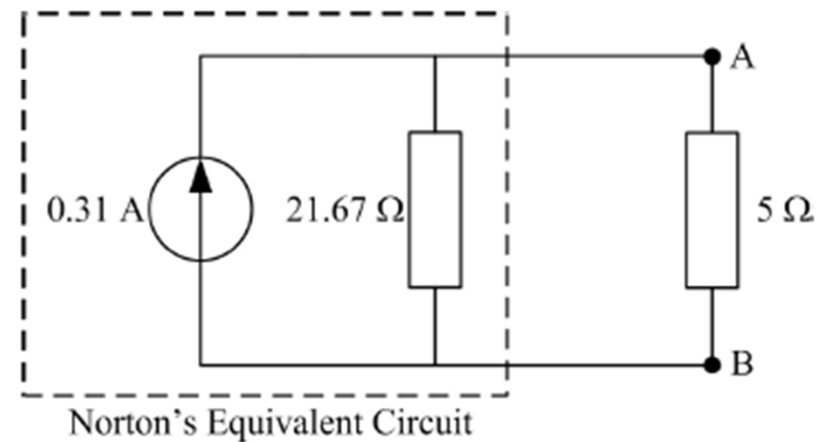

A current source unlike a voltage source is not a physical reality


## Filters:

To modify the parts (frequencies) of a signal


- Active (amplifiers)
- Passive (only reduction / removal of certain freqs)

Passive : Combinations of R, L & C

Types:

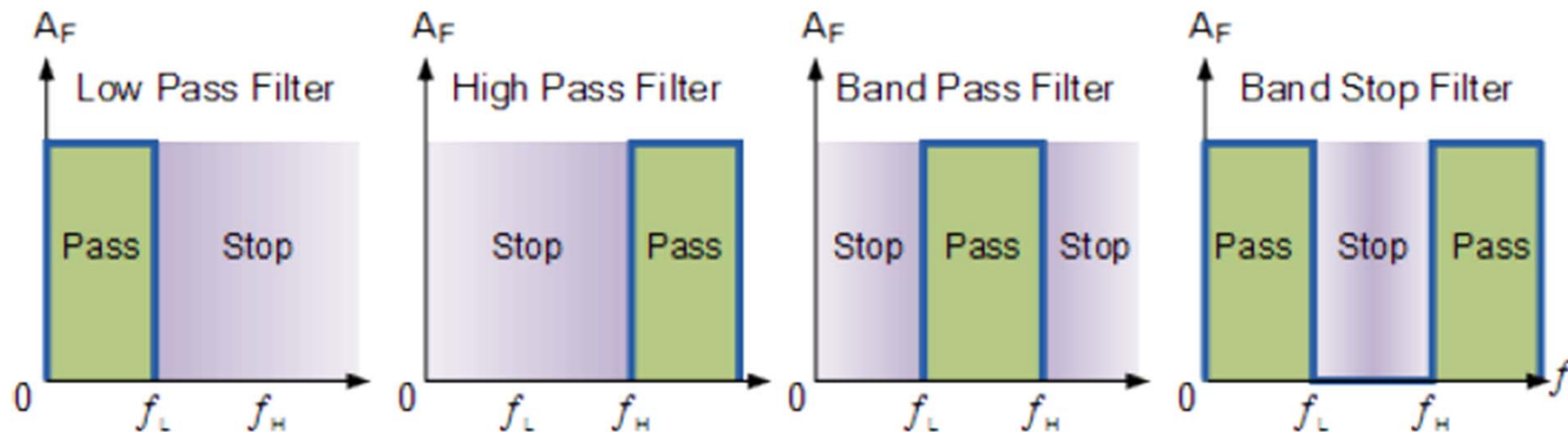

## LPF

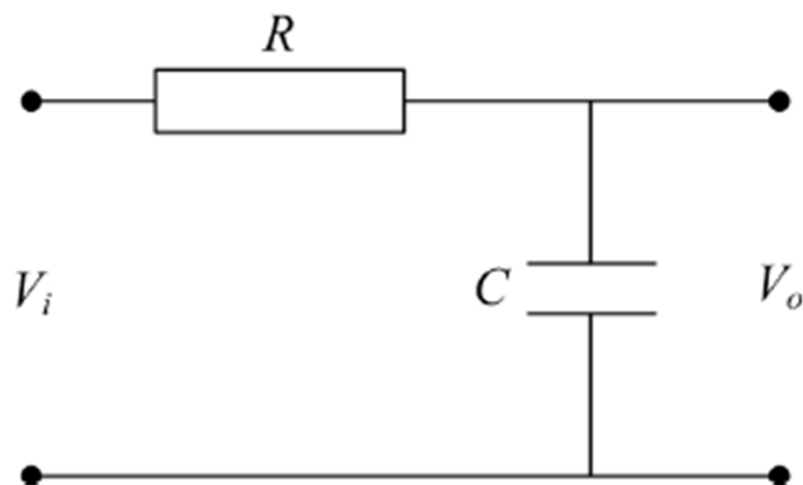


$$V_o = V_i \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$


$$V_o = V_i \frac{1}{1 + j\omega RC}$$

$$H(j\omega) = \frac{V_o}{V_i} = \frac{1}{1 + j\omega T} \quad T = RC$$

$$A = |H(j\omega)| = \frac{1}{\sqrt{1 + (\omega T)^2}} \quad A_{dB} = 20 \log_{10} A$$

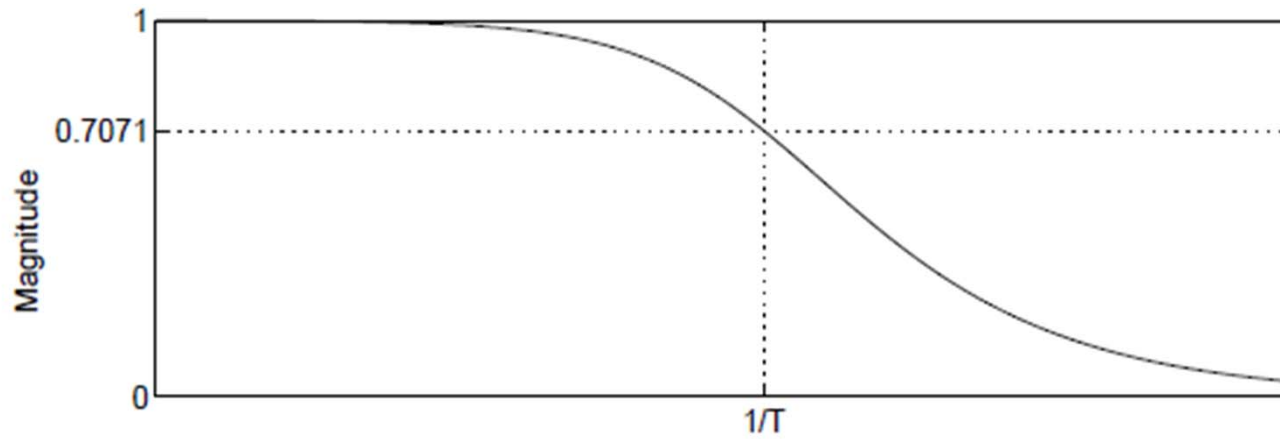
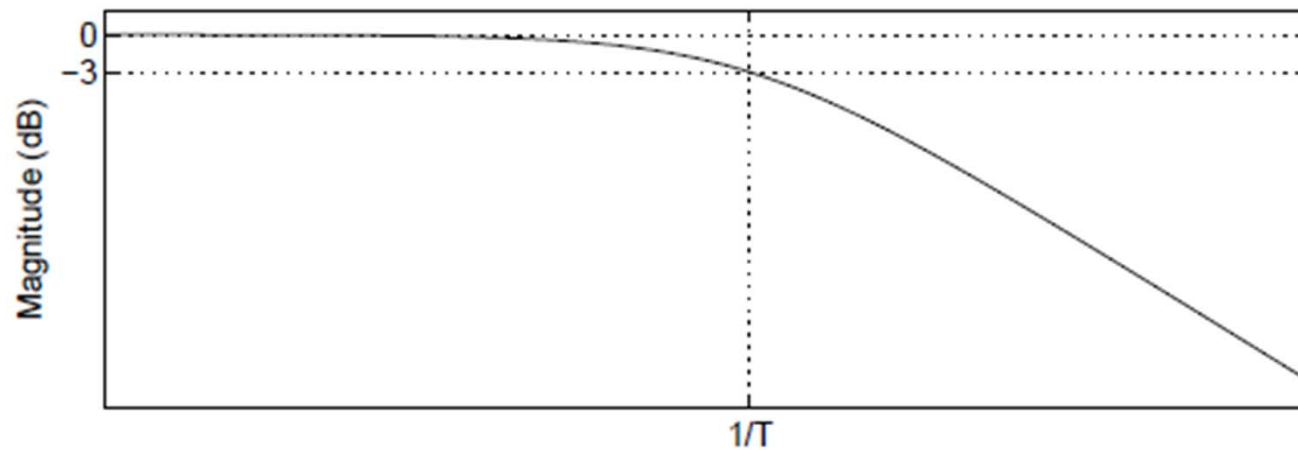
$$A \geq \frac{1}{\sqrt{2}} \rightarrow \omega = \text{Bandwidth} = \frac{1}{T} = \frac{1}{RC}$$



$$A \rightarrow |V_o| = |V_i| \frac{X_c}{\sqrt{R^2 + X_c^2}}$$





# Charging - discharging

Charging  $V(t) = V_0(1 - e^{-t/\tau})$



Discharging  $V(t) = V_0(e^{-t/\tau})$


$$\tau = RC$$

RC small & large

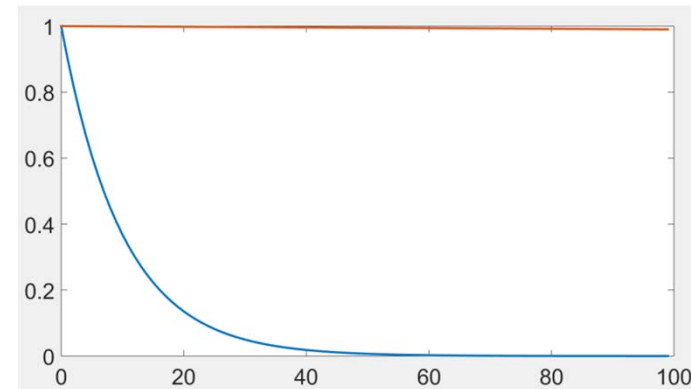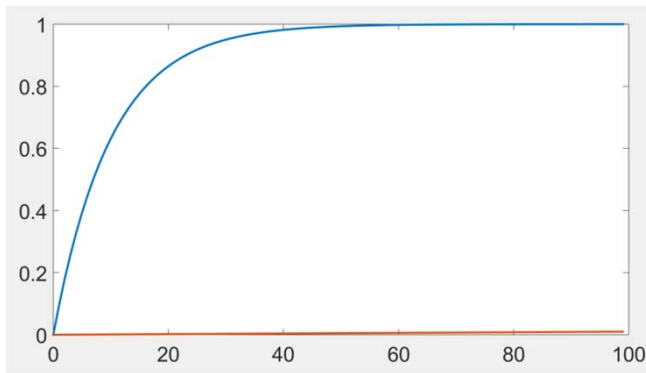

RC large

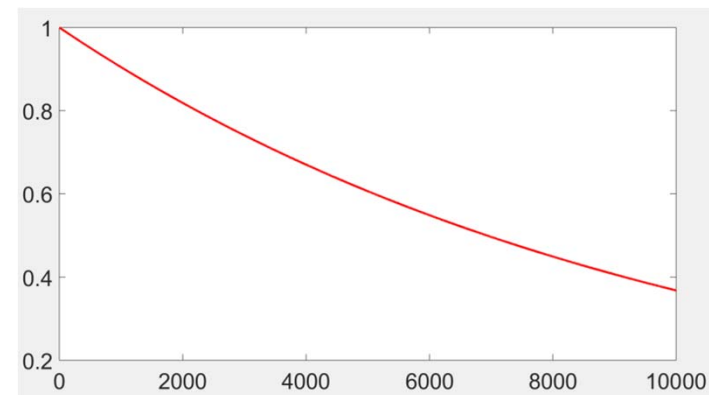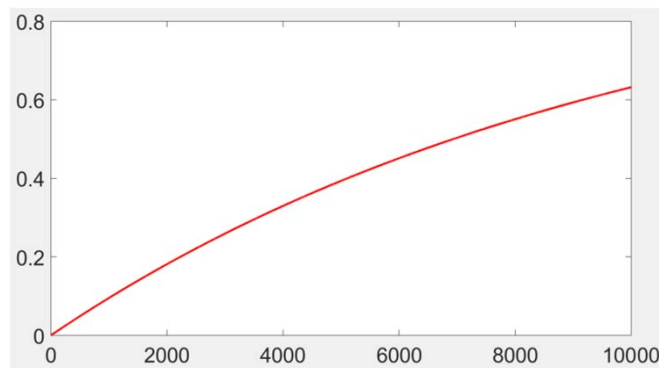


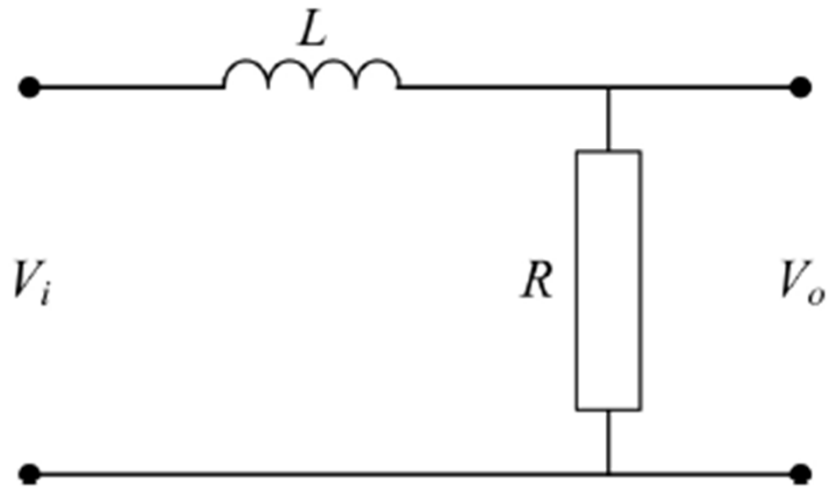


$$V_o = V_i \frac{R}{R + j\omega L}$$

$$T = \frac{L}{R} \quad |V_o| = |V_i| \frac{R}{\sqrt{R^2 + X_L^2}}$$


**HPF**

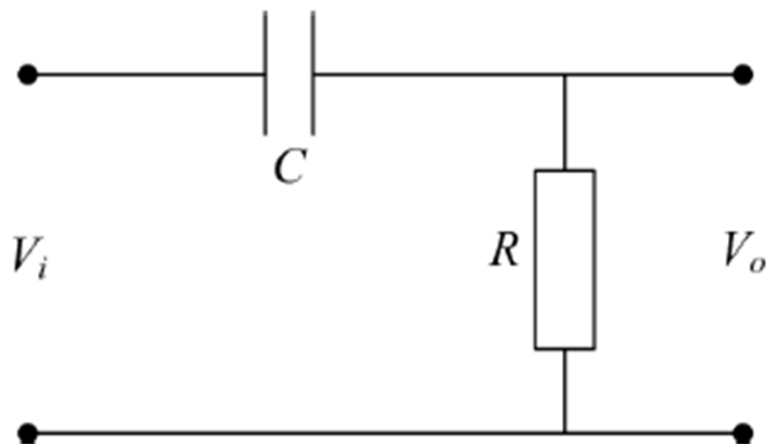
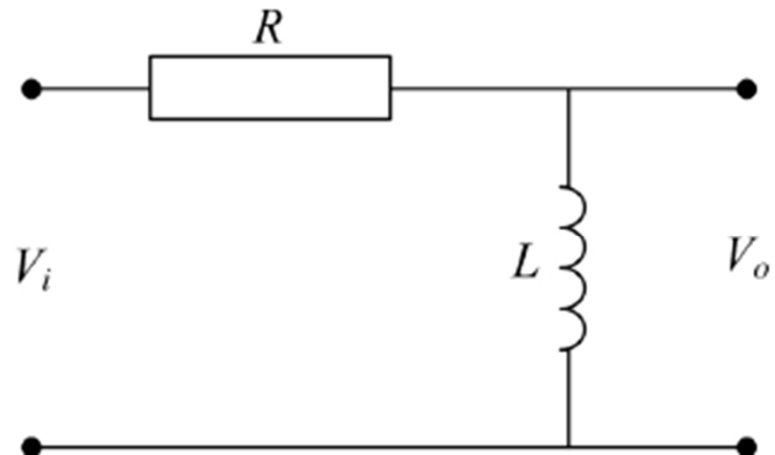
$$\frac{V_o}{V_i} = \frac{1}{1 + \frac{1}{j\omega RC}}$$



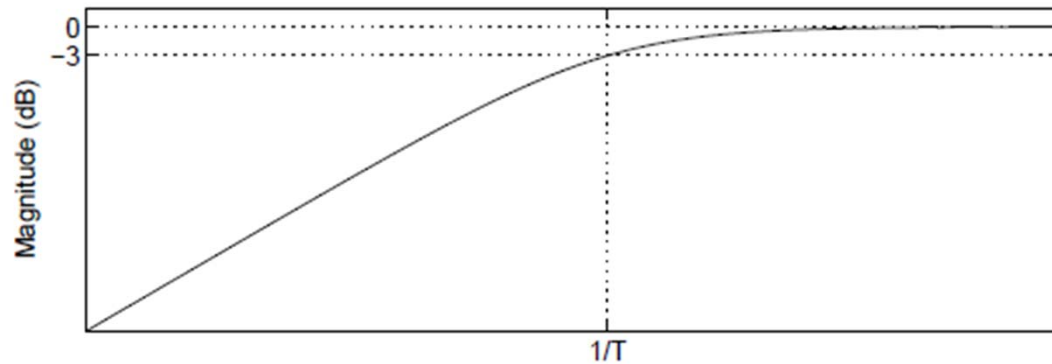
$$\frac{V_o}{V_i} = \frac{1}{1 + \frac{R}{j\omega L}}$$



$$\omega = 1/T$$

Cut-off

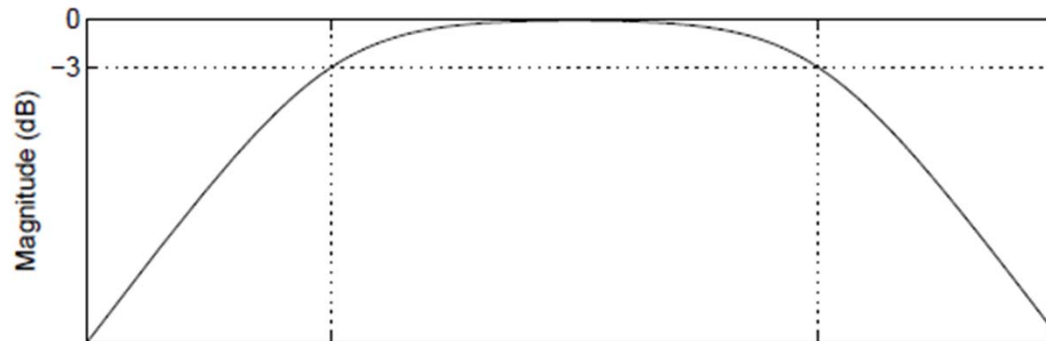**BPF  $\rightarrow$  LPF (small RC) – LPF (large RC)  
or HPF (large RC) – LPF (small RC)**



**BSF  $\rightarrow$  LPF (large RC) + HPF (small RC)**

## Pulse response:

