

# **DC Analysis of Transistor Circuits**

## DC analysis procedure:

For DC analysis, knowledge of mode of operation of the transistor is required. Sometimes Guess to Start!

- Assume transistor in forward-active mode,  
 $V_{BE} = V_{BE}(\text{on})$ ,  $I_B > 0$  and  $I_C = \beta I_B$ .
- If analysis proves  $I_B < 0$  and  $V_{CE} < V_{CE}(\text{sat})$  then assumption is wrong, restart.


$$I_C / I_B < \beta$$

$$\frac{I_C}{I_B} \equiv \beta_{\text{Forced}}$$

$$\beta_{\text{Forced}} < \beta$$

Biased in Saturation mode  
(both forward bias)


## Example (tutorial):

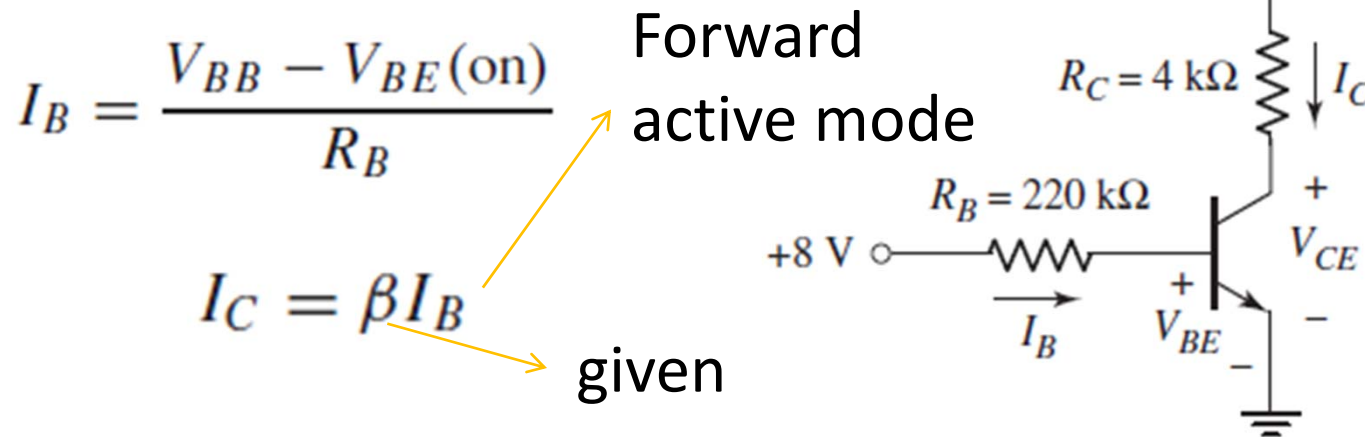

$$V_{CE} = V_{CC} - I_C R_C \Rightarrow \text{Negative } (< V_{CE(\text{Sat})})$$

$$I_C = I_C(\text{sat}) = \frac{V_{CC} - V_{CE(\text{sat})}}{R_C} \rightarrow \text{given} \quad \frac{I_C}{I_B} < \beta$$

4 modes

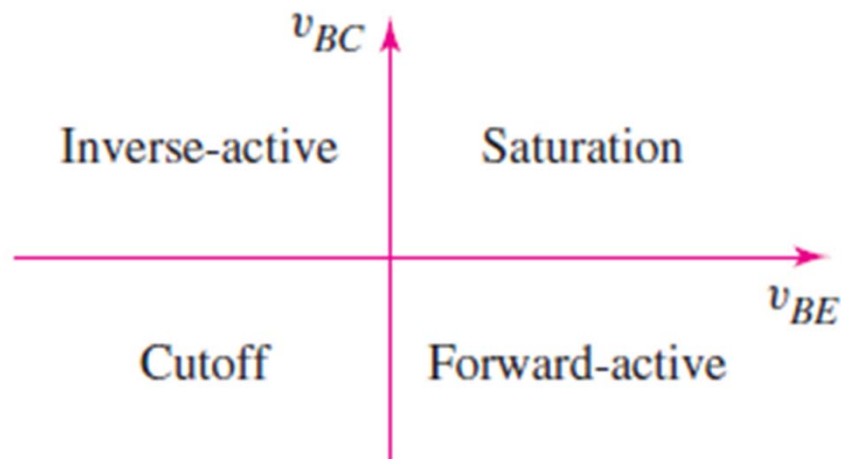

## Inverse-active mode:


B–E junction is reverse biased and the B–C junction is forward biased.

- The transistor is operating “upside down”, emitter acting as a collector and collector as an emitter
- Transistors are not electrically & physically symmetrical, so it will have significantly smaller  $\beta$
- BJTs have very low saturation voltage (mV)
- App: Digital Electronics Circuit


Piecewise linear model  $\leftrightarrow$  Ebers-Moll model

## Voltage Transfer Characteristics:

Output voltage versus input voltage

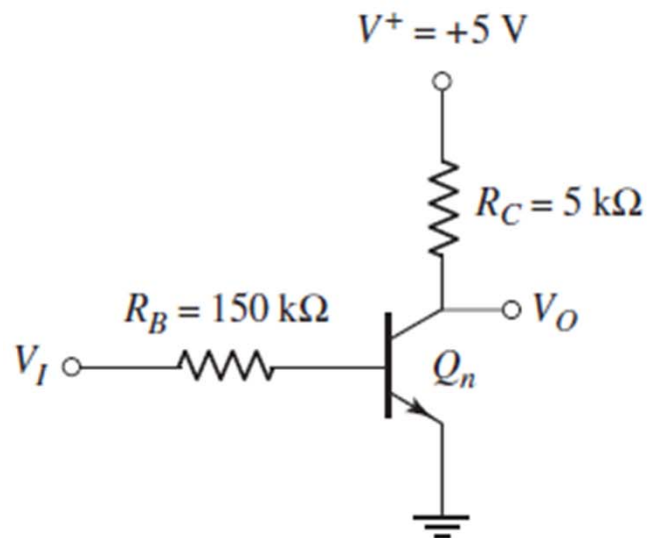
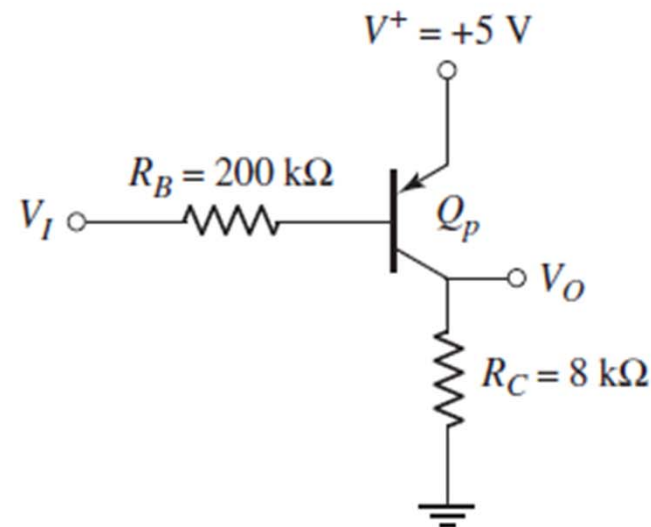
$$V_{BE}(on) = 0.7\text{ V}, \beta = 120, \\ V_{CE}(sat) = 0.2\text{ V}, V_A \rightarrow \infty$$



$$V_{EB}(on) = 0.7\text{ V}, \beta = 80, \\ V_{EC}(sat) = 0.2\text{ V}, V_A \rightarrow \infty$$

## NPN

$$I_B = \frac{V_I - 0.7}{R_B}$$


$$V_I \leq 0.7 \text{ V}, \quad I_B = I_C = 0, \quad V_O = V^+ = 5 \text{ V}.$$

$$V_I > 0.7 \text{ V}, \quad I_C = \beta I_B = \frac{\beta(V_I - 0.7)}{R_B}$$

$$V_O = 5 - I_C R_C = 5 - \frac{\beta(V_I - 0.7)R_C}{R_B}$$

$$V_O = V_{CE} \quad V_O = 0.2 \text{ V} \quad V_I = 1.9 \text{ V}.$$
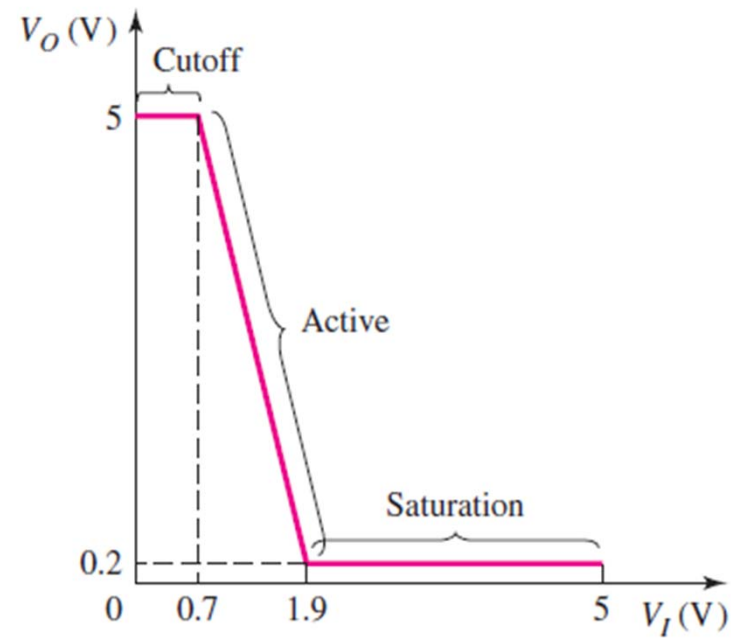
$$V_I \geq 1.9 \text{ V} \quad V_O = 0.2 \text{ V}.$$



PNP

$$4.3 \leq V_I \quad I_B = I_C = 0 \quad V_O = 0$$


$$V_I < 4.3 \text{ V}, \quad I_B = \frac{(5 - 0.7) - V_I}{R_B} \quad I_C = \beta I_B = \beta \left[ \frac{(5 - 0.7) - V_I}{R_B} \right]$$

$$V_O = I_C R_C = \beta R_C \left[ \frac{(5 - 0.7) - V_I}{R_B} \right]$$

$$V^+ - V_O = V_{EC} \quad V_O = 4.8 \text{ V}, \quad V_I = 2.8 \text{ V}.$$

$$V_I \leq 2.8 \text{ V},$$

$$V_O = 4.8 \text{ V},$$

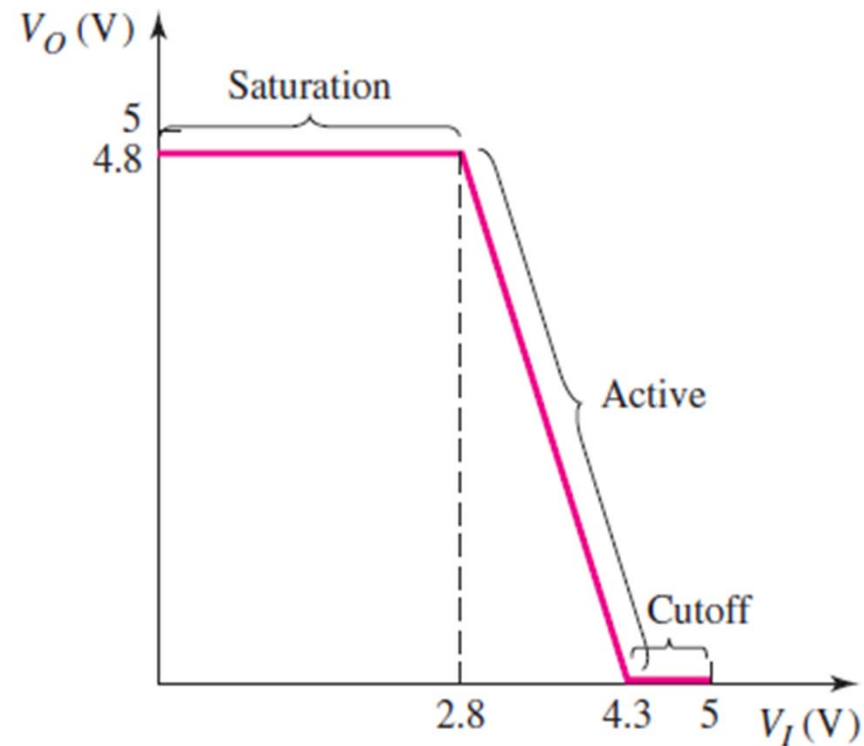


Voltage transfer characteristics are determined by finding the **range of input voltage** values that biases the transistor in **cut off, the forward-active mode, or the saturation mode**.



# **Basic Transistor Applications**

# Switch:

## Inverter

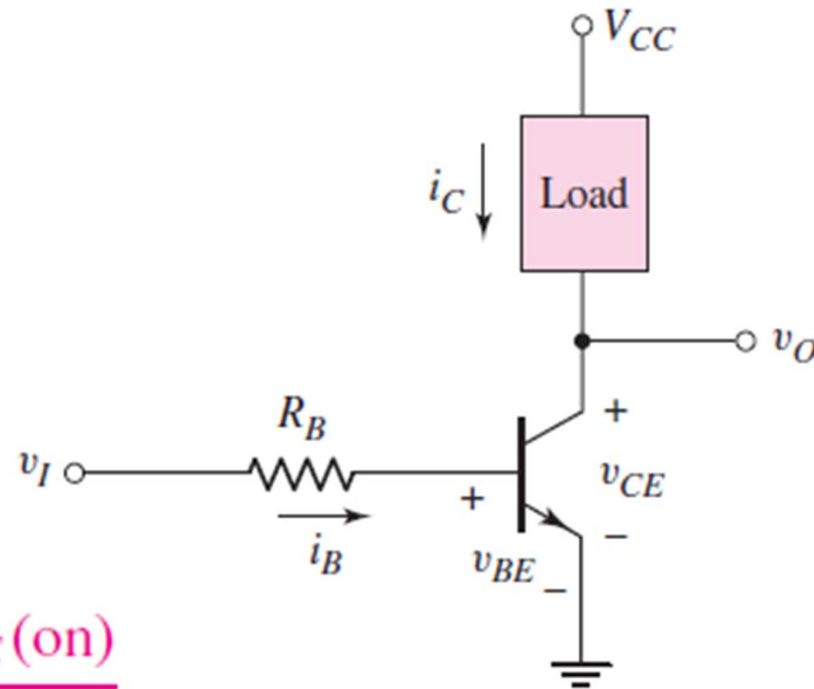

$$i_B \cong \frac{v_I - V_{BE}(\text{on})}{R_B}$$

$$v_I < V_{BE}(\text{on})$$

$$i_B = i_C = 0$$

$$v_O = V_{CC}$$


$$v_I = V_{CC}$$

$$\frac{R_B}{R_C} < \beta \rightarrow \text{saturation mode}$$

$$i_C = I_C(\text{sat}) = \frac{V_{CC} - V_{CE}(\text{sat})}{R_C}$$

$$v_O = V_{CE}(\text{sat})$$

# Digital Logic

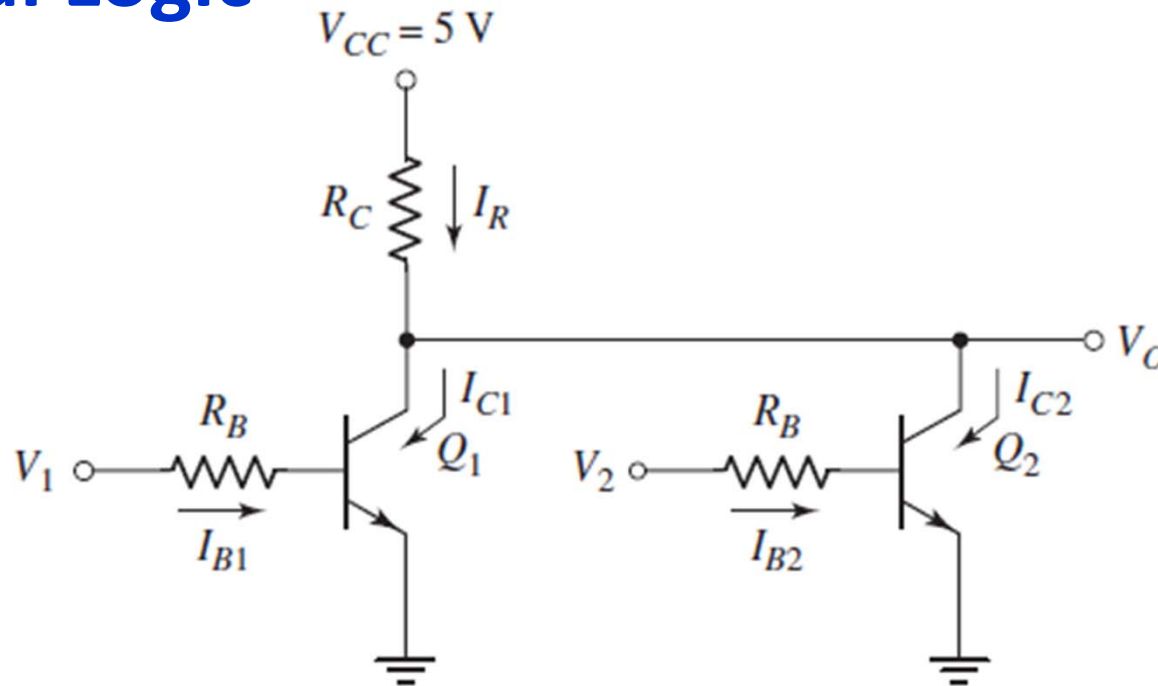

**$V_1 = 0, V_2 = 0 \rightarrow V_O = 5V$ , both cut off**

**$V_1 = 5, V_2 = 0 \rightarrow V_O = 0.2V$ , Q1 saturation Q2 cut off**

**$V_1 = 0, V_2 = 5 \rightarrow V_O = 0.2V$ , Q2 saturation Q1 cut off**


**$V_1 = 5, V_2 = 5 \rightarrow V_O = 0.2V$ , Q1 saturation Q2saturation**

## Positive logic system - NOR logic function

- Bipolar transistor circuits can be configured to perform **logic functions**
- Logic circuits must be designed to minimize or **eliminate** such **loading effects**

The bipolar NOR logic circuit response		
$V_1$ (V)	$V_2$ (V)	$V_o$ (V)
0	0	5
5	0	0.2
0	5	0.2
5	5	0.2

# Amplifier

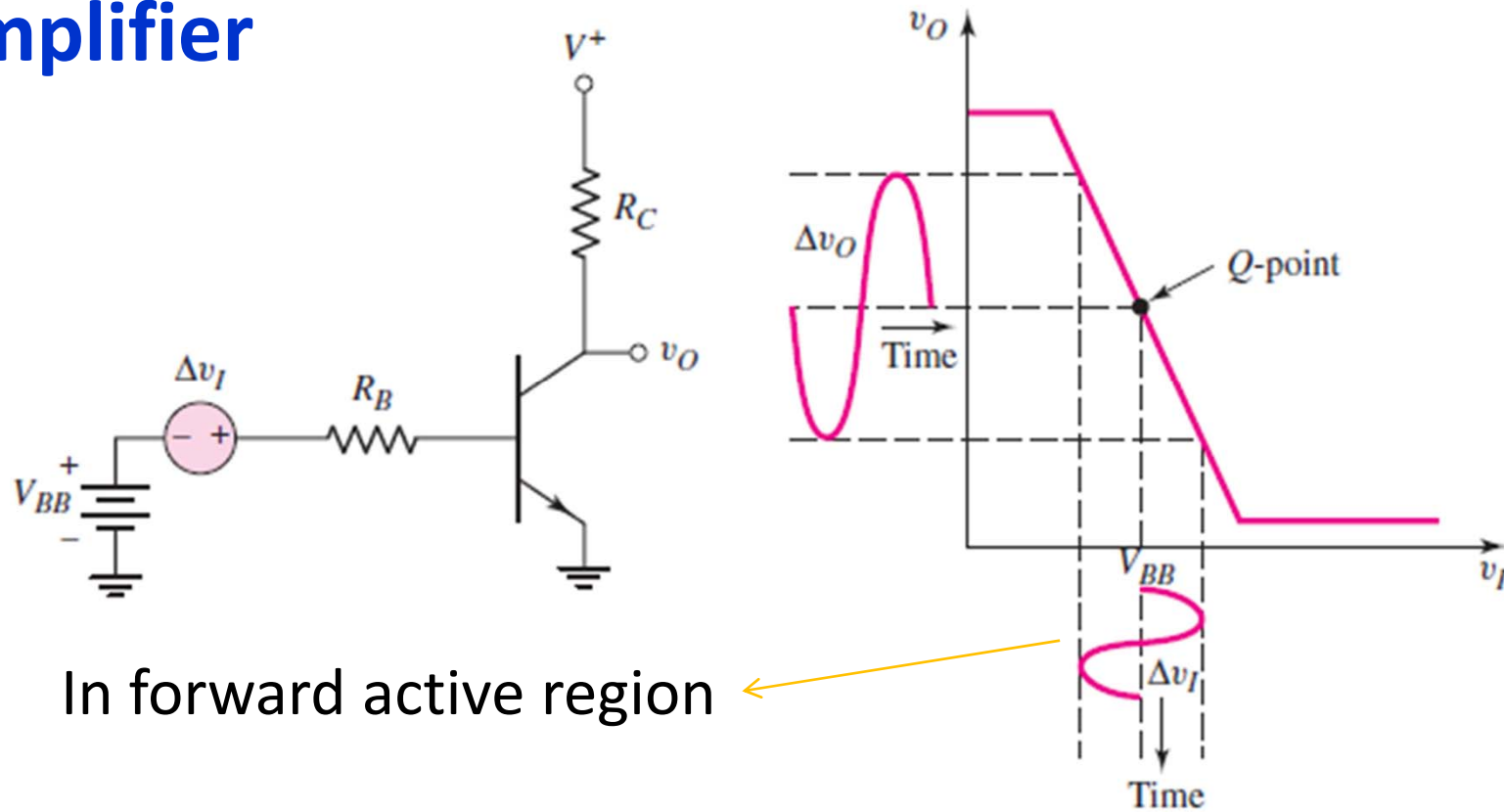


In forward active region

$$v_O = V^+ - I_C R_C = V^+ - \frac{\beta(V_{BB} + \Delta v_I - 0.7)}{R_B} R_C$$

$$V_O + \Delta v_O = V^+ - \frac{\beta(V_{BB} - 0.7)}{R_B} R_C - \frac{\beta \Delta v_I}{R_B} R_C$$

Therefore, the bipolar inverter circuit with **proper biasing** can be used to amplify a **time-varying signal**.

Improper DC biasing:

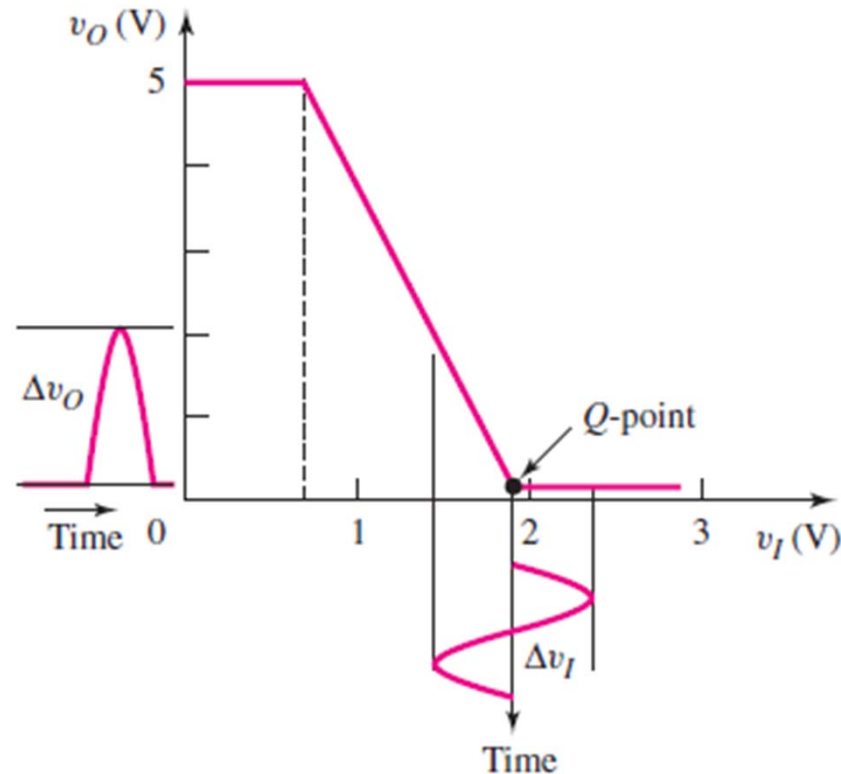

There are **many schemes** for properly biasing the transistor for analog or amplifier applications