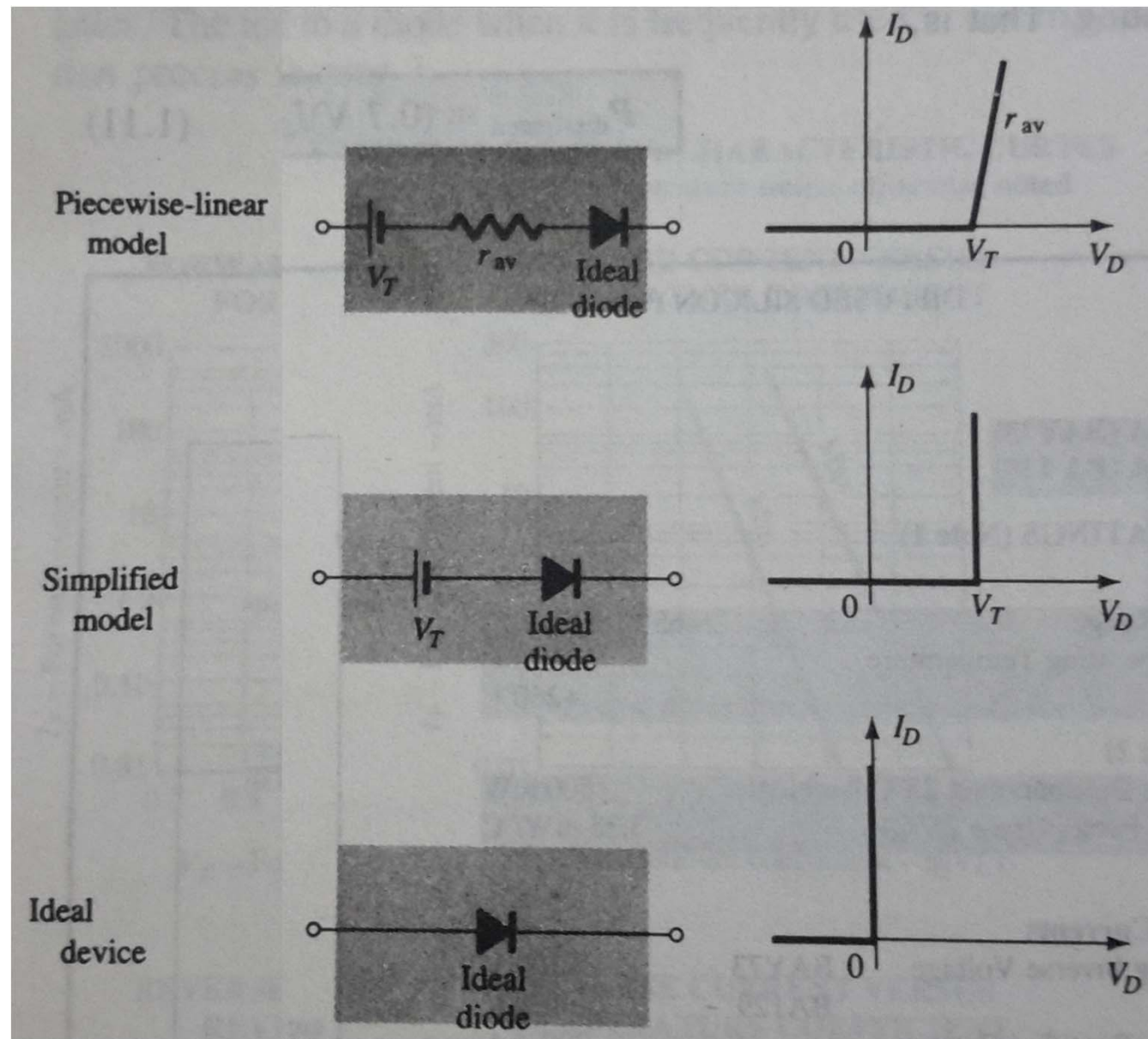


Diode circuits – AC equivalent

Diode equivalents & approximations:





GOAL:

Develop an equivalent circuit for a diode that is used when a small, time-varying signal is applied to a diode circuit.


Why? - because **sinusoidal signals** may be **superimposed** on the **dc currents** and **voltages**

Sinusoidal Analysis

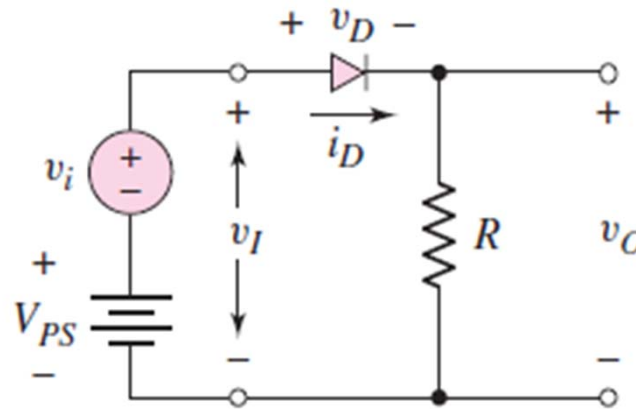

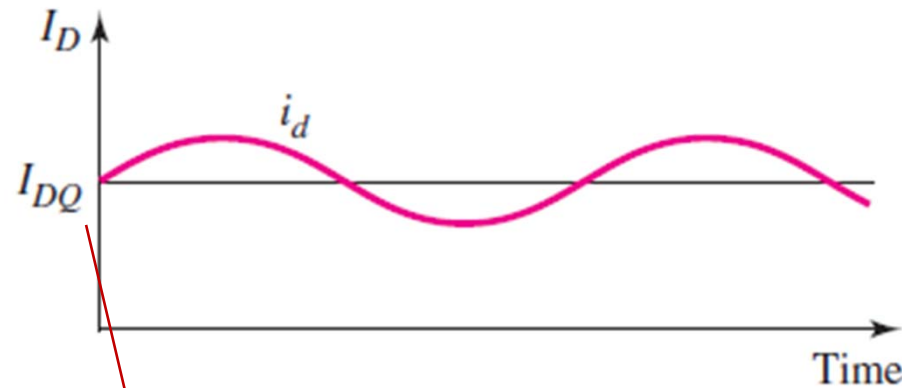

quiescent (Q)
diode current
& voltage

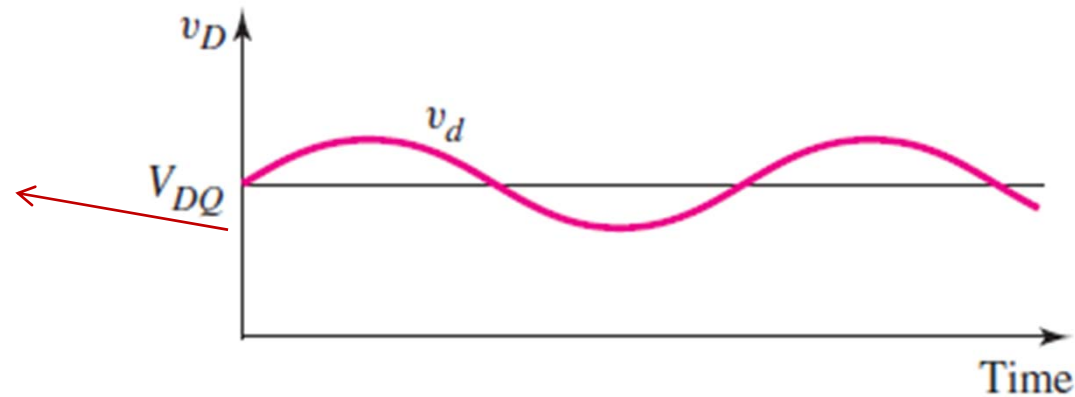

Input voltage contains a **dc component** with an **ac signal superimposed**

Diode current and diode voltage will also be so.

$$i_D \cong I_S e^{\left(\frac{v_D}{V_T}\right)} = I_S e^{\left(\frac{V_{DQ} + v_d}{V_T}\right)} \quad \text{"-1 term neglected"}$$

$$i_D = I_S \left[e^{\left(\frac{V_{DQ}}{V_T}\right)} \right] \cdot \left[e^{\left(\frac{v_d}{V_T}\right)} \right]$$



If the ac signal is "small," then $v_d \ll V_T$

$$e^{\left(\frac{v_d}{V_T}\right)} \cong 1 + \frac{v_d}{V_T}$$

$$I_{DQ} = I_S e^{\left(\frac{V_{DQ}}{V_T}\right)}$$

$$i_D = I_{DQ} \left(1 + \frac{v_d}{V_T} \right) = I_{DQ} + \frac{I_{DQ}}{V_T} \cdot v_d = I_{DQ} + i_d$$

 additive

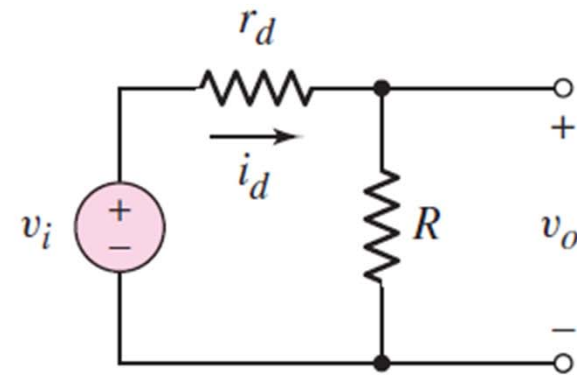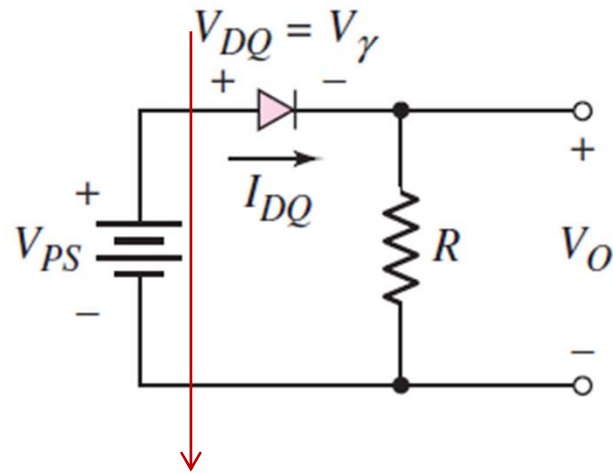

Diode resistance
very small

$$i_d = \left(\frac{I_{DQ}}{V_T} \right) \cdot v_d = g_d \cdot v_d$$

or

$$v_d = \left(\frac{V_T}{I_{DQ}} \right) \cdot i_d = r_d \cdot i_d$$

$$r_d = \frac{1}{g_d} = \frac{V_T}{I_{DQ}}$$


A dc analysis involving only the dc voltages and currents, and an ac analysis involving only the ac voltages and currents

Small-signal **incremental conductance and resistance**, also called the **diffusion conductance and diffusion resistance**

Incremental resistance is a function of the dc bias current I_{DQ} and is inversely proportional to the slope of the I–V characteristics curve


$$v_d = \left(\frac{V_T}{I_{DQ}} \right) \cdot i_d$$

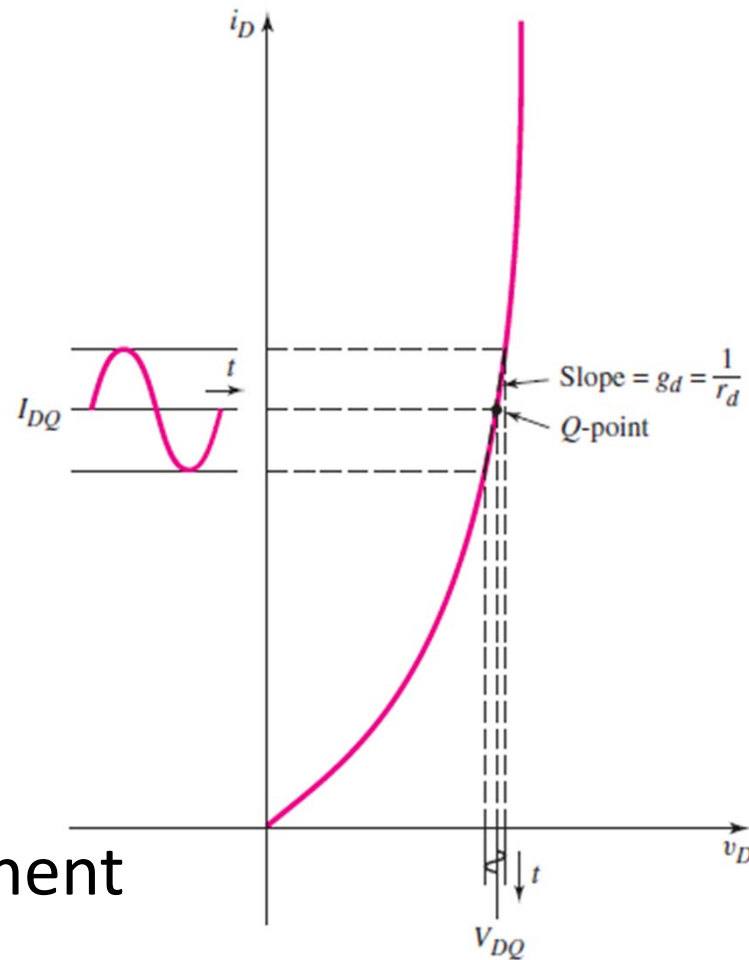Represents the changing voltage & current component



Circuit Analysis:

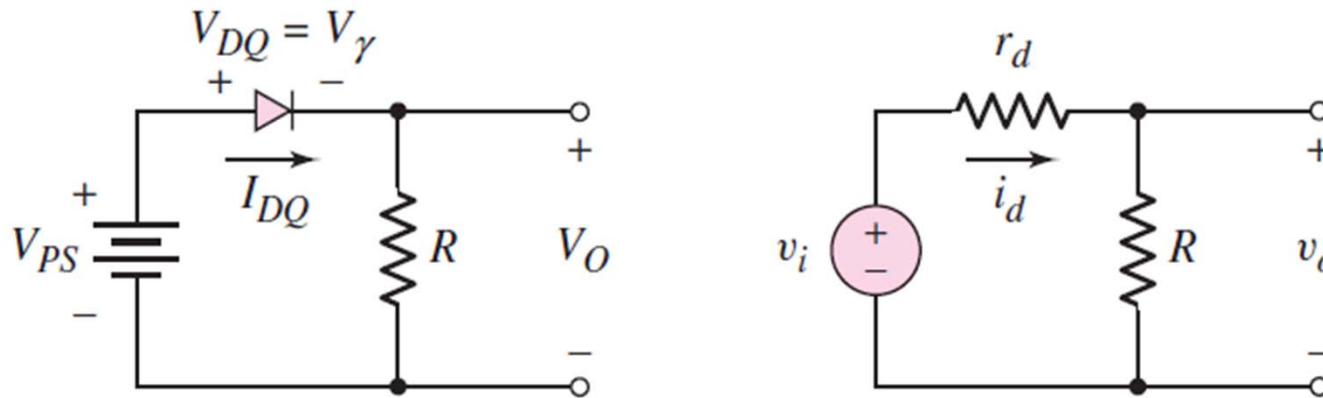First perform a dc analysis and then an ac analysis



If the diode is forward biased, then the voltage across the diode is the piecewise linear turn-on voltage

The diode has been replaced by its equivalent resistance. All parameters are small-signal time-varying parameters

Assume circuit and diode parameters of $V_{PS} = 5 \text{ V}$, $R = 5 \text{ k}\Omega$, $V_\gamma = 0.6 \text{ V}$, and $v_i = 0.1 \sin(\omega t) \text{ V}$.

DC analysis –

$$I_{DQ} = \frac{V_{PS} - V_\gamma}{R} = \frac{5 - 0.6}{5} = 0.88 \text{ mA}$$

$$V_o = I_{DQ}R = (0.88)(5) = 4.4 \text{ V}$$

AC analysis –

$$v_i = i_d r_d + i_d R = i_d (r_d + R)$$


$$r_d = \frac{V_T}{I_{DQ}} = \frac{0.026}{0.88} = 0.0295 \text{ k}\Omega$$

$$i_d = \frac{v_i}{r_d + R} = \frac{0.1 \sin \omega t}{0.0295 + 5} \Rightarrow 19.9 \sin \omega t \text{ } (\mu\text{A})$$

$$v_o = i_d R = 0.0995 \sin \omega t \text{ (V)}$$

Frequency response:

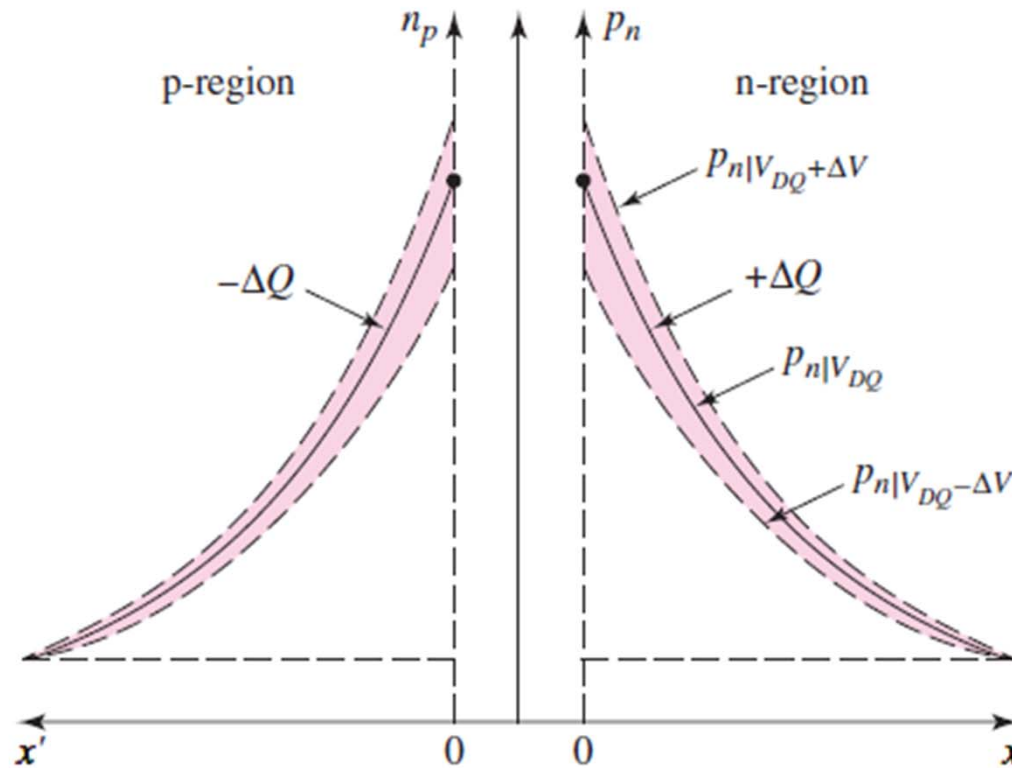- Frequency of the ac signal was small enough that capacitance effects in the circuit would be negligible.
- If the frequency of the ac input signal increases, the diffusion capacitance associated with a forward-biased pn junction becomes important



Fluctuations in diffused minority concentration


The $+\Delta Q$ charge is alternately being charged and discharged through the pn junction as the voltage across the junction changes.

$$C_d = \frac{dQ}{dV_D}$$

The **diffusion capacitance** is normally much **larger** than the **junction capacitance**.


Small-Signal Equivalent Circuit:

$$g_d + j\omega C_d$$

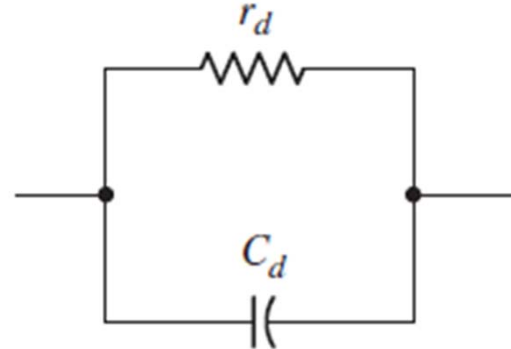

Simplified

Complete

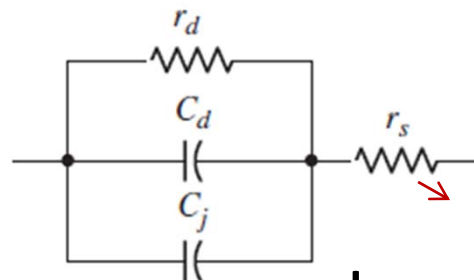


→ Neutral region resistance

→ Junction capacitance

Other Diodes!

Other Diode Types:

Solar Cell (photodiode)

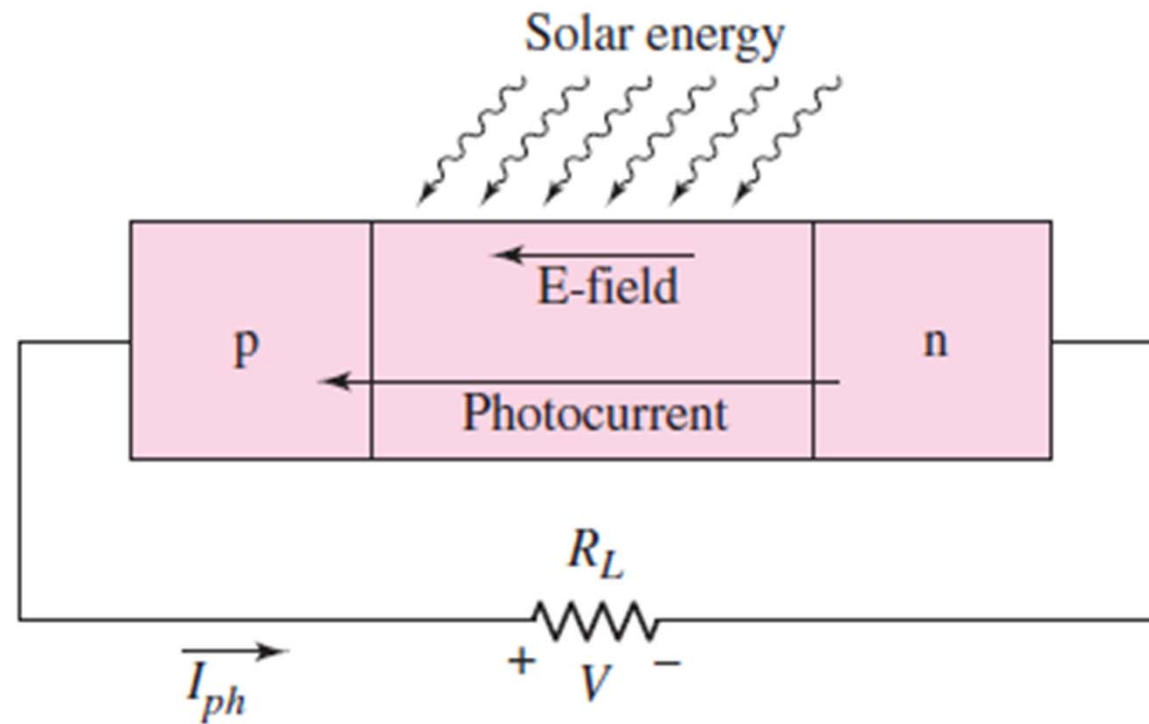




GaAs or Si

Light Emitting Diode (LED):

GaAs – direct band gap –

Useful as LED

Si – indirect band gap – not useful

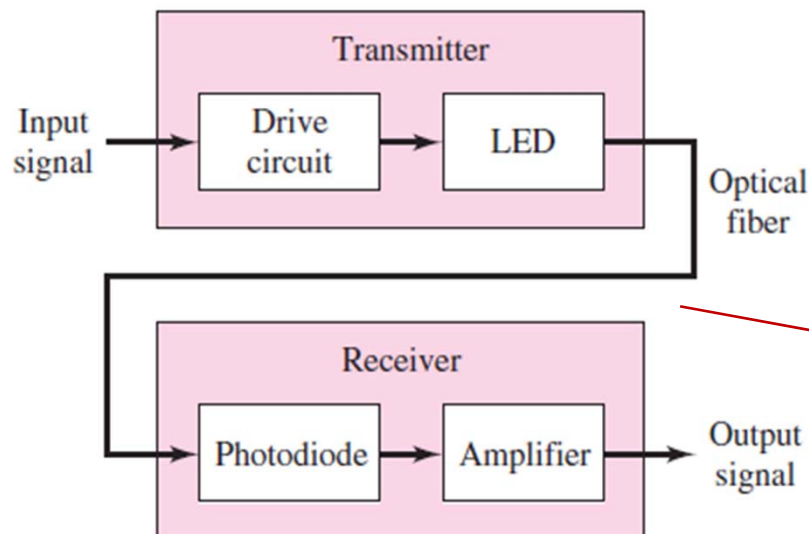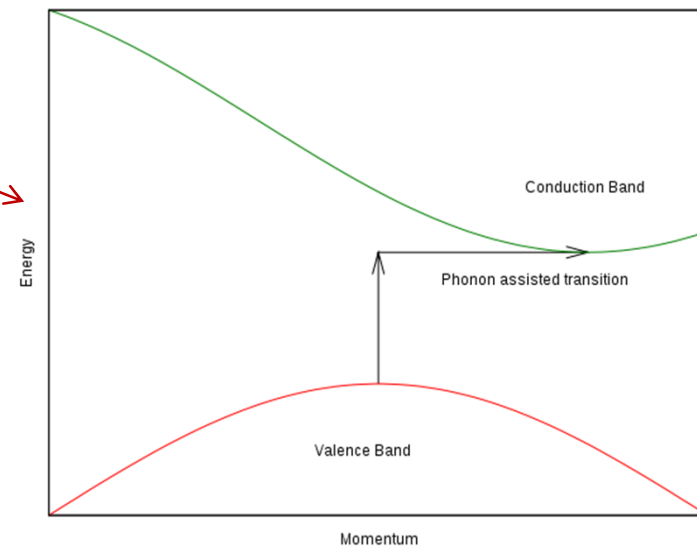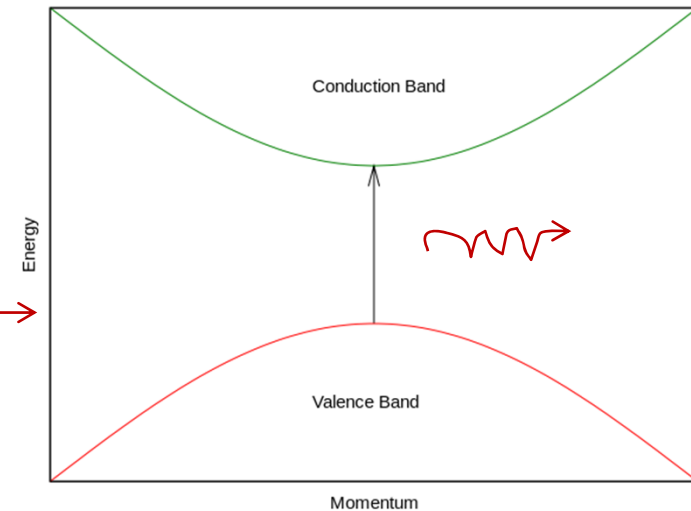

optical transmission system

Schottky diode:




A **metal** (like Al) is brought into contact with a moderately doped **n-type semiconductor**

Current in a Schottky diode results from the **flow of majority carriers** over the **potential barrier** (+ive ion in n-type and excess electrons in metal). **Electrons** are **majority** both in **n-type** and **metal**.

Forward bias effects **similar** to **pn-junction**, but the **barrier** is much **lesser**. **Reverse bias** results in **larger saturation current** due to substantial amount of **electrons** in **metal**.

Adv:

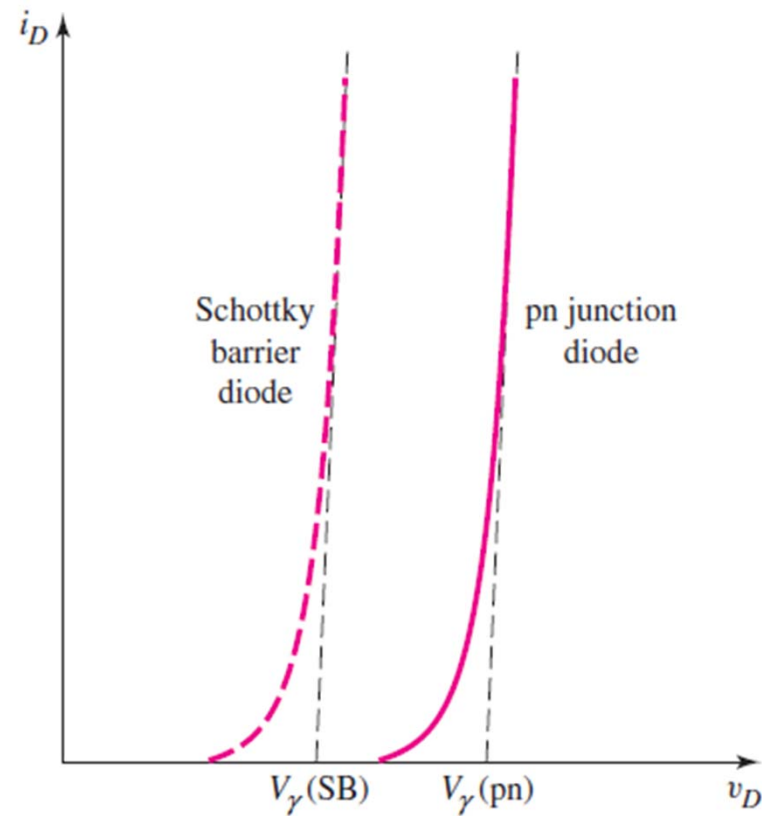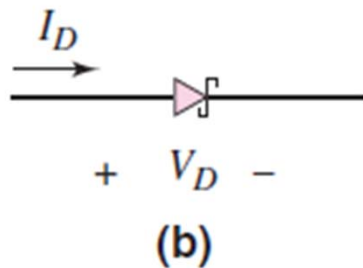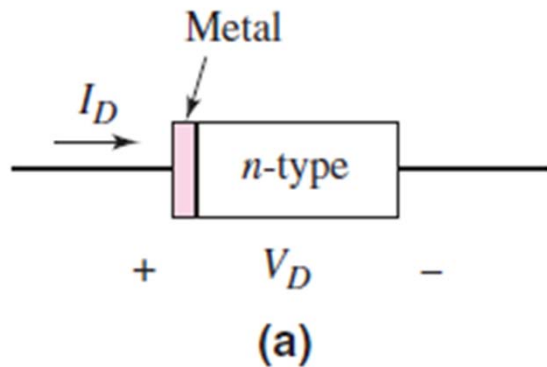Because there is no excess minority carrier accumulation, **switching** from on to off is **much faster**.






Zener diode:

When **reversed bias voltage** is increased, at some point (breakdown voltage) **breakdown occurs** and the reverse bias **current increases rapidly**.

Zener diodes are fabricated to have a specified breakdown voltage V_{z0} , **Zener potential / Zener breakdown voltage**. The **large current** can be **limited** (otherwise catastrophic failure can occur).

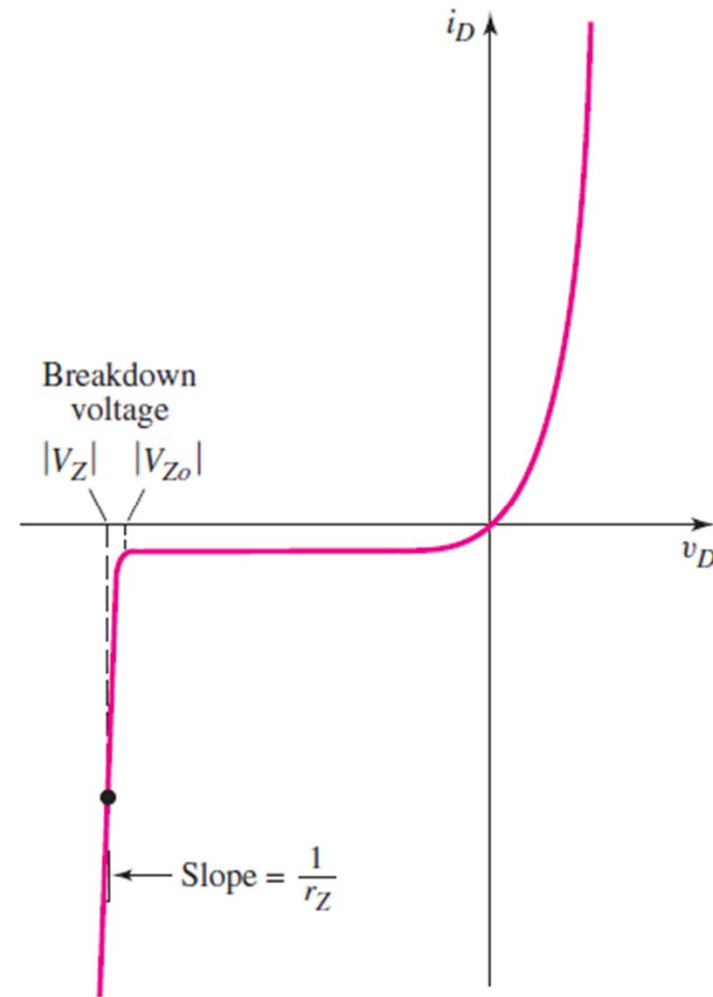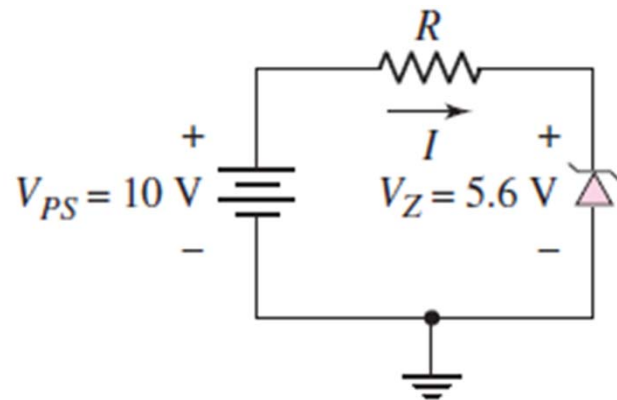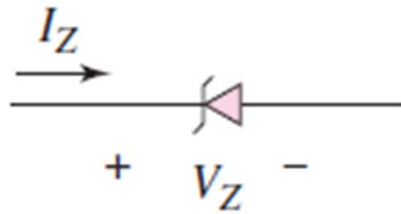Such a diode can be used as a **constant-voltage reference** in a circuit. The diode **breakdown voltage** is essentially **constant** over a wide range of **currents** and **temperatures**.




Current restriction
to 3 mA

$$R = \frac{V_{PS} - V_Z}{I} = \frac{10 - 5.6}{3} = 1.47 \text{ k}\Omega$$


Diode circuits – Rectifier circuits

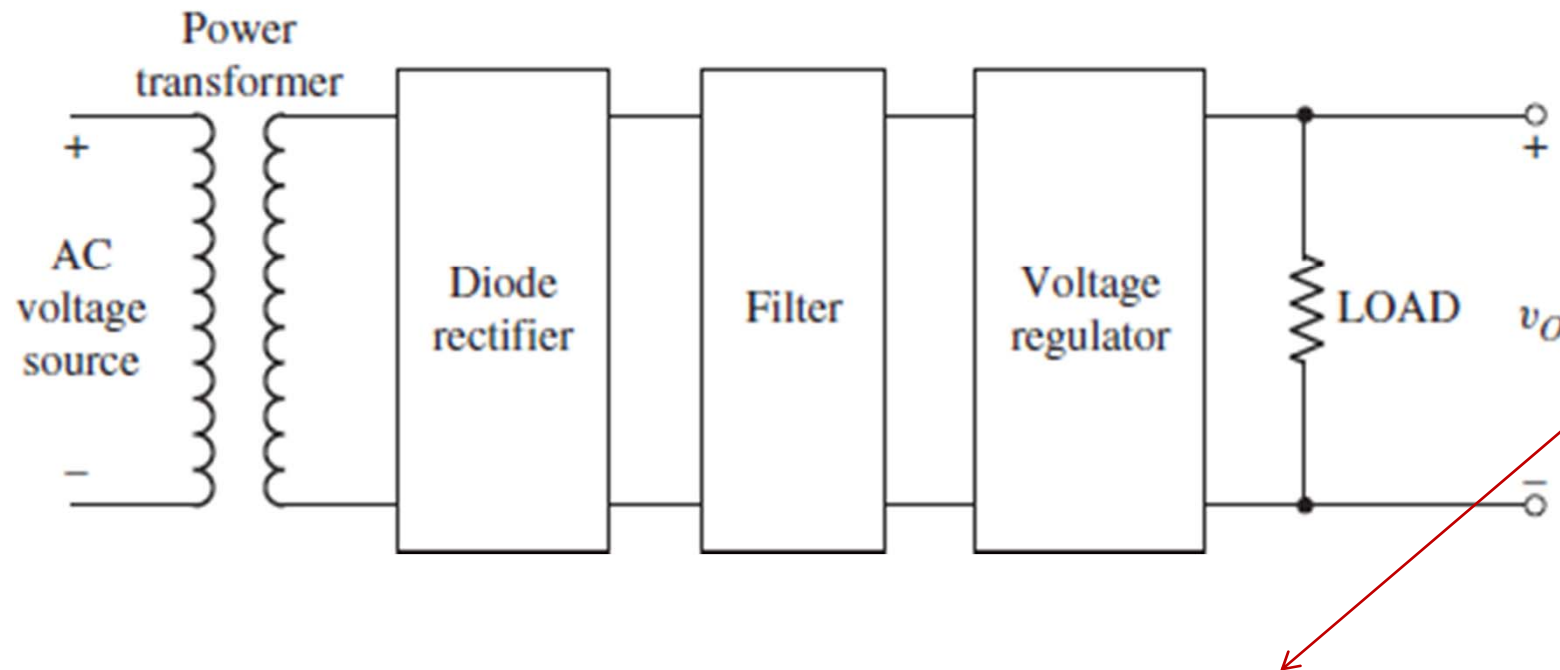A diode rectifier forms the first stage of a dc power supply, which is required in any kind of electronic device



Usually 3V to 24V

Half-Wave Rectification:

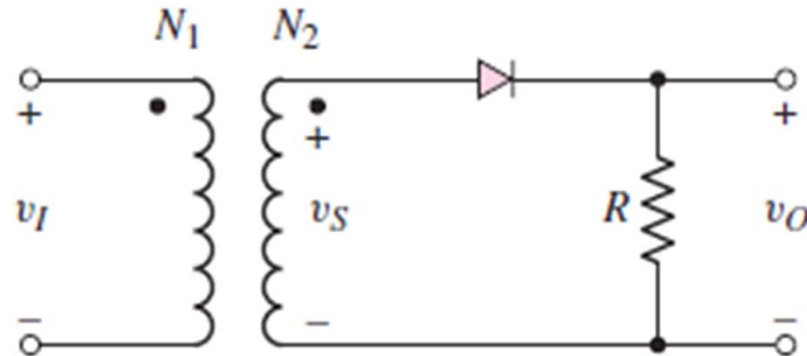


We use the **piecewise linear approach** in analyzing this circuit, assuming the diode **forward resistance is 0**.

$$\text{RMS AC voltage} \leftarrow \frac{v_I}{v_S} = \frac{N_1}{N_2} \longrightarrow \text{transformer turns ratio}$$

Desired relation between input and output of the rectifier circuit

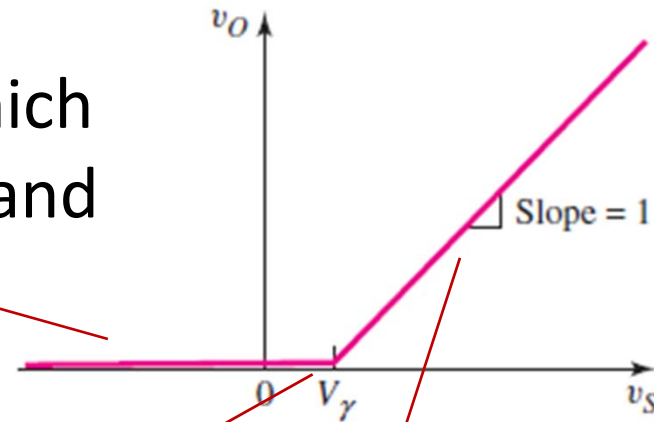The diode is **reverse biased**, which means that the current is zero and the **output voltage is zero**.



The diode will be **non-conducting**, so the output voltage will **remain zero**.


The diode is **forward biased** and a **current is induced** in the circuit.

$$i_D = \frac{v_S - V_\gamma}{R}$$


$$v_O = i_D R = v_S - V_\gamma$$

When v_s is sinusoidal, the output v_o is also the same. But it is zero when v_s is less than V_γ , otherwise it is

$$v_O = v_S - V_\gamma$$


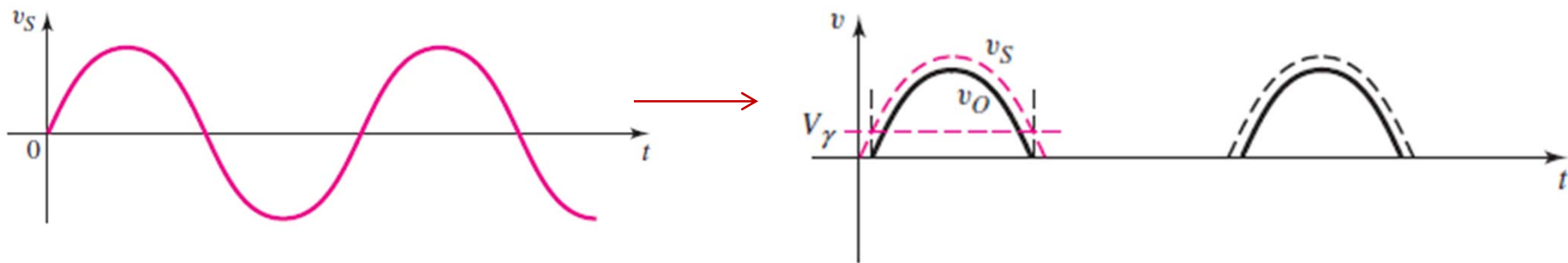


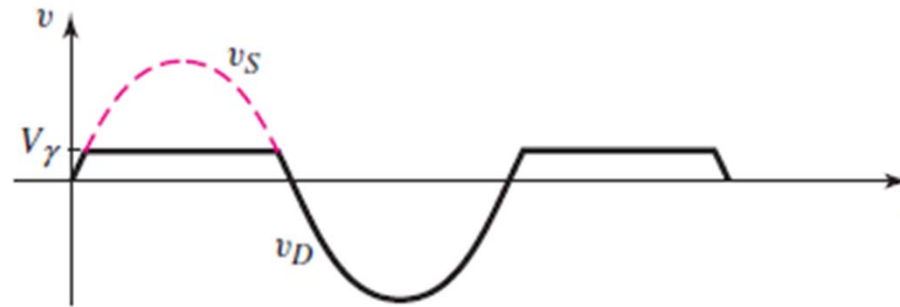Since the output voltage appears only during the **positive cycle of the input signal**, the circuit is called a **half-wave rectifier**.



The diode must be capable of **handling the peak current** in the forward direction and sustaining the largest **peak inverse voltage (PIV)** without breakdown.

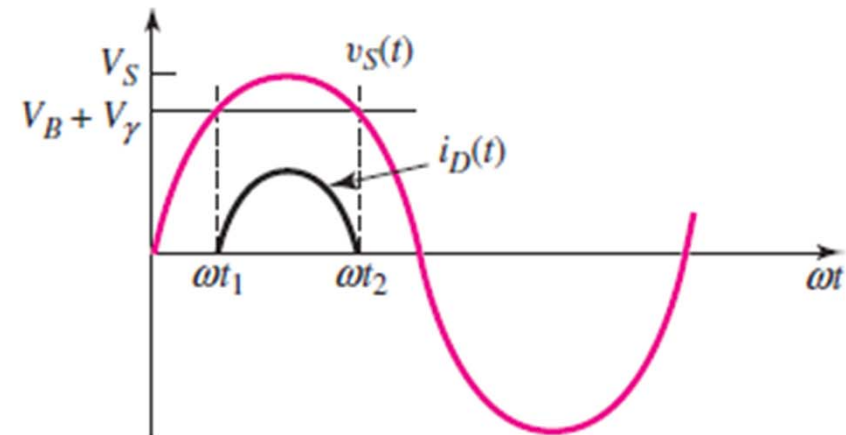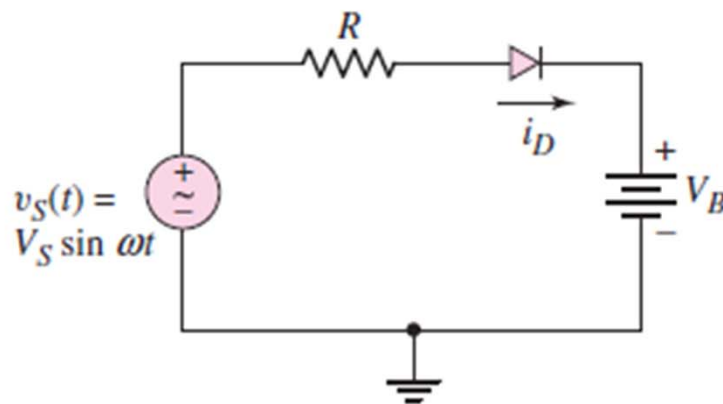
Half-wave rectifier circuit to charge a battery



- Charging current exists whenever the instantaneous ac source voltage is greater than the battery voltage plus the diode cut-in voltage.
- The resistance R in the circuit is to limit the current.
- Thus current flows only in the direction to charge the battery as it is zero when the AC voltage is less than V_B .

Disadvantage of the half-wave rectifier is that we “waste” the negative half-cycles.


Full-Wave Rectification:

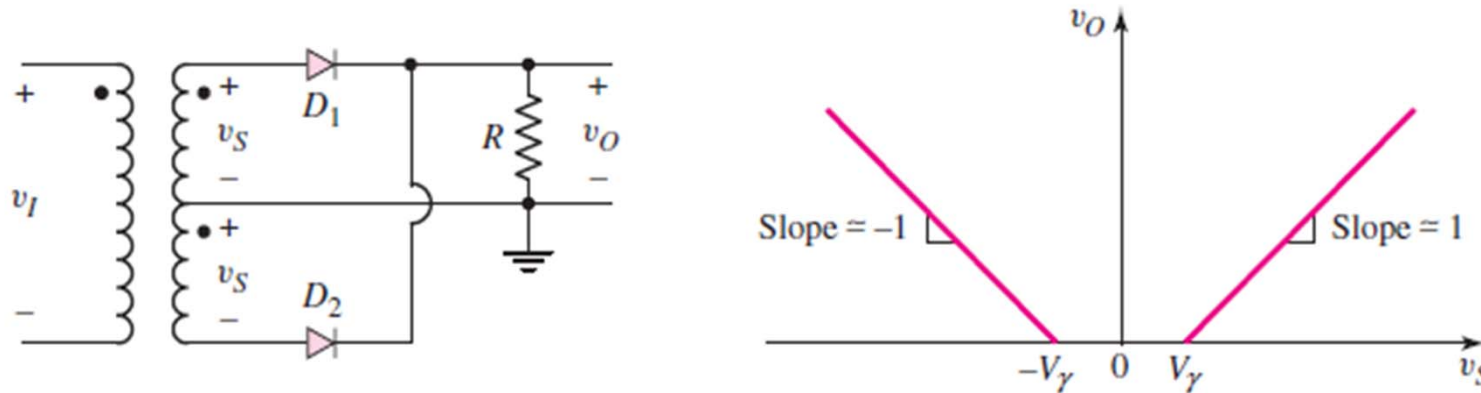

The output $v_o = v_s - V_\gamma$ when v_s is greater than V_γ with D_1 open and D_2 off.

The output $v_o = -v_s - V_\gamma$ when v_s is lesser than $-V_\gamma$ with D_2 open and D_1 off.

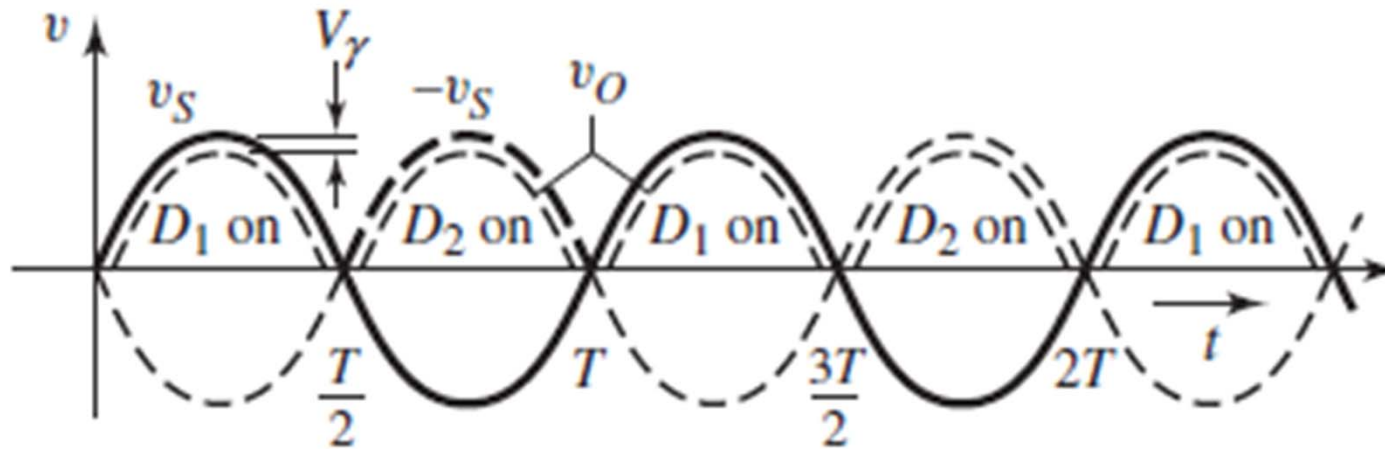
The output $v_o = 0$ when $-V_\gamma < v_s < V_\gamma$ with both D_1 & D_2 closed.




Since a rectified **output voltage occurs** during both the **positive** and **negative cycles** of the **input signal**, this circuit is called a **full-wave rectifier**.

Bridge rectifier


2 more diodes but no center tapping!

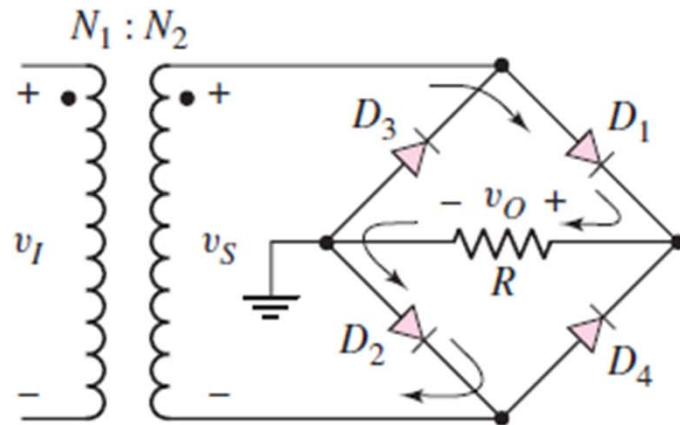


Secondary not grounded!

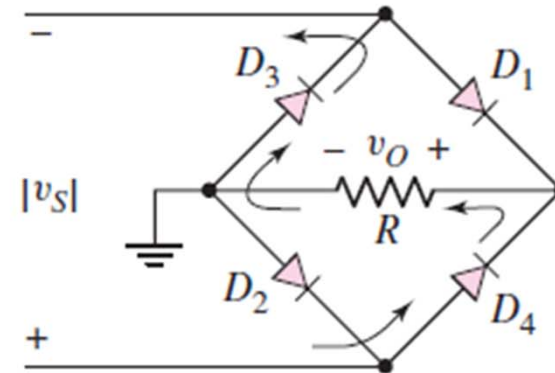

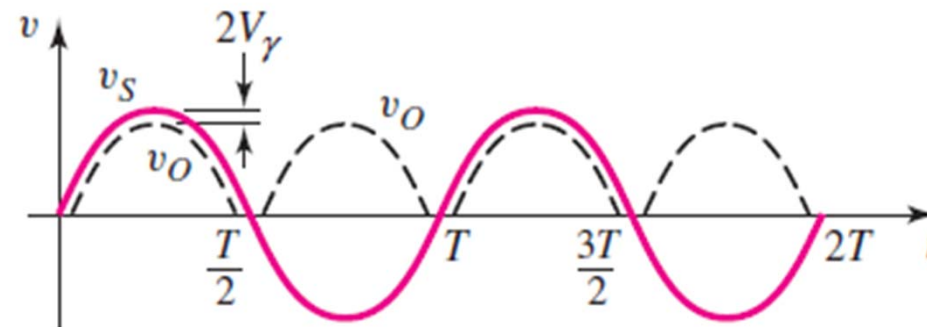- During **positive half** of the cycle, only **D1 and D2** are open and during the **negative half** of the cycle only **D3 and D4** are open.
- The magnitude of v_O is **two diode drops** less than the magnitude of v_S




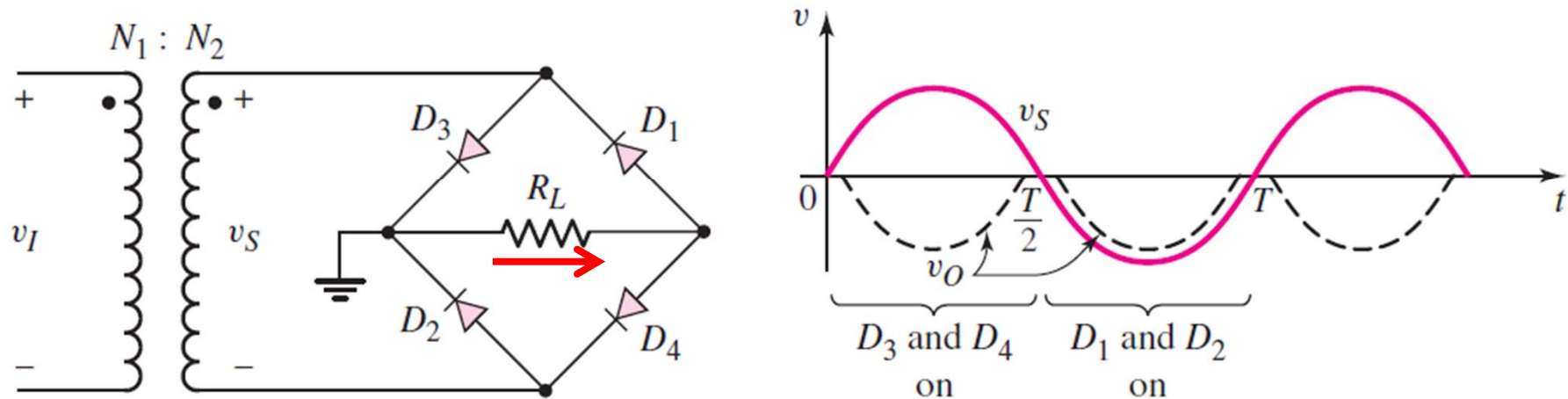There are times when a negative dc voltage is also required. We can produce negative rectification by reversing the direction of the diodes in either circuit




- During **positive half** of the cycle, only **D3 and D4** are open and during the **negative half** of the cycle only **D1 and D2** are open.

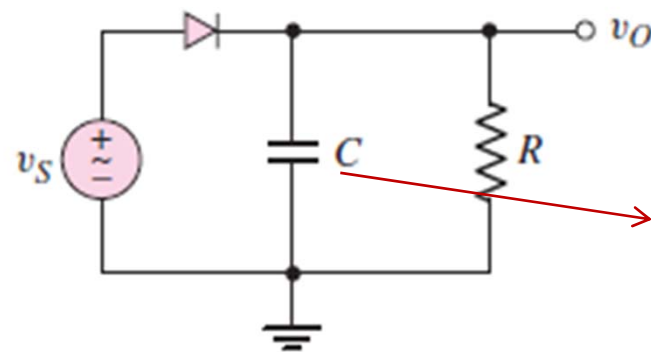
Filters, Ripple Voltage, and Diode Current




Filter capacitor

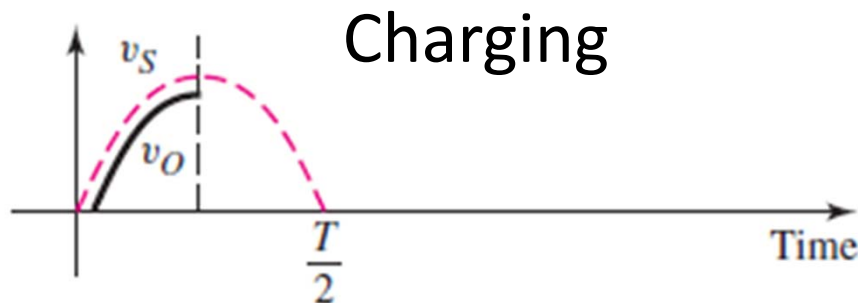

Charging

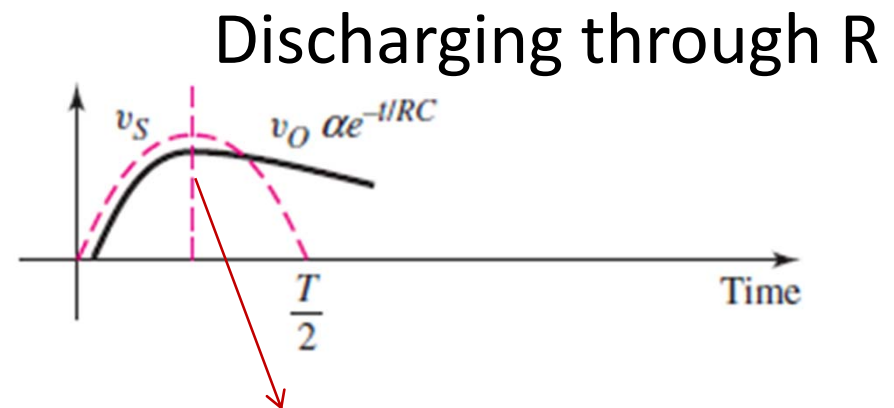


Discharging through R

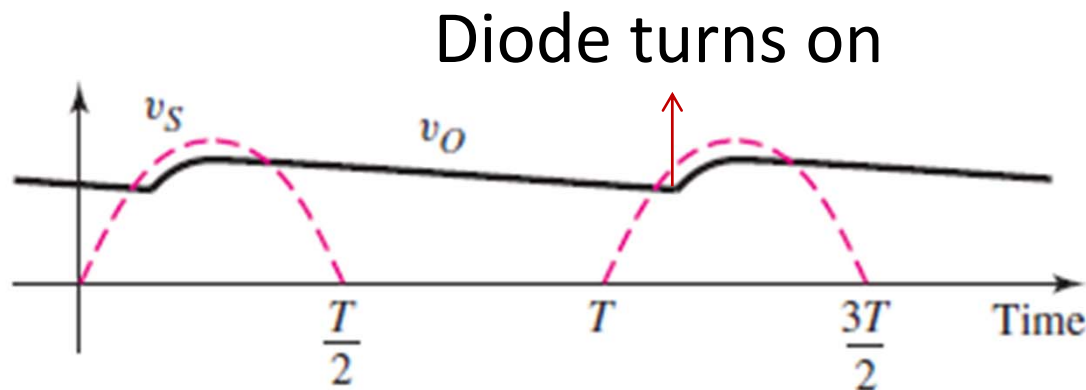

Diode turns on


Diode turns off almost after peak, as difference between input voltage and capacitor discharge voltage is less the cut-in

For full-wave rectifier

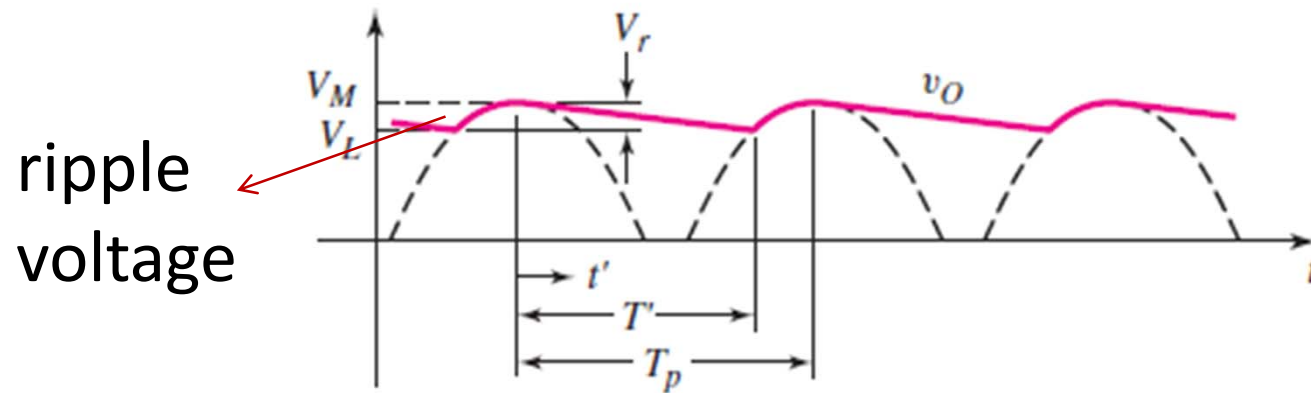

ripple voltage

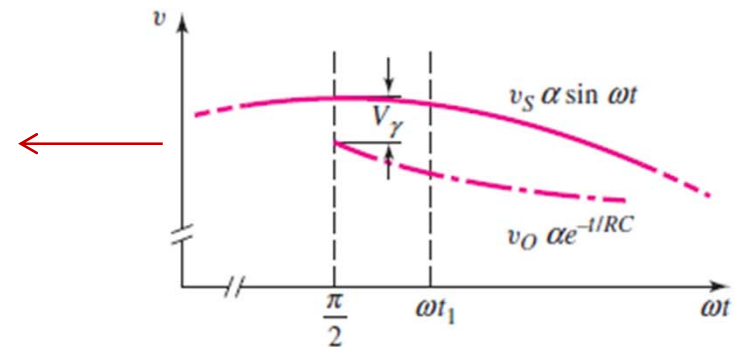Diode turns off a little while after peak



$$v_O(t) = V_M e^{-t'/\tau} = V_M e^{-t'/RC}$$

Smallest o/p voltage

$$V_L = V_M e^{-T'/RC}$$

Ripple voltage $V_r = V_M - V_L = V_M(1 - e^{-T'/RC})$

$$T' \ll RC \quad e^{-T'/RC} \cong 1 - \frac{T'}{RC}$$

$$V_r \cong V_M \left(\frac{T'}{RC} \right) \longrightarrow \text{depends on RC!}$$

If ripple effect is small -


$$T' = T_p \quad V_r \cong V_M \left(\frac{T_p}{RC} \right)$$

For full wave rectification $f = \frac{1}{2T_p}$ Half-wave $f = \frac{1}{T_p}$

$$V_r = \frac{V_M}{2fRC}$$

Full-wave rectifier has
half the ripple voltage of
the half-wave rectifier


Consider ideal diode:

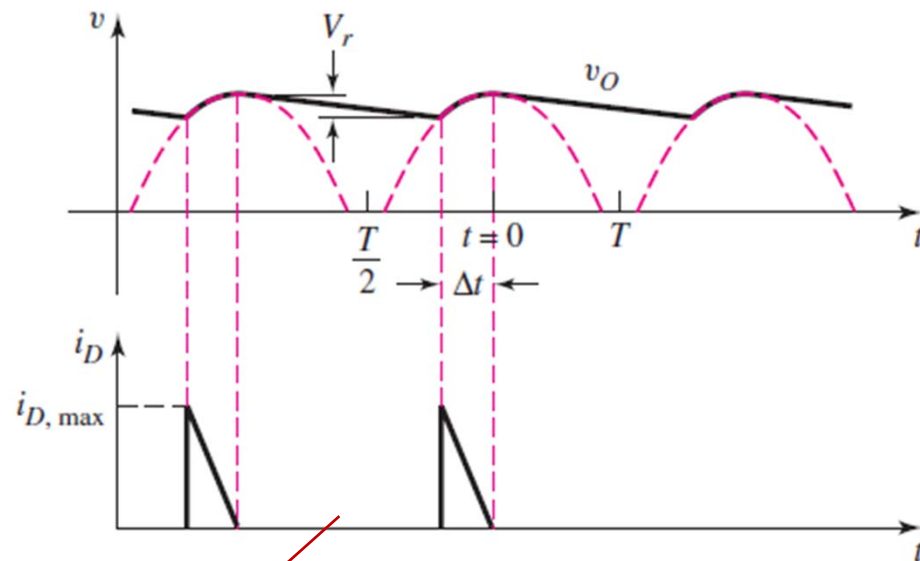

(a) diode conduction time

(b) diode current

Similar for
capacitor
current

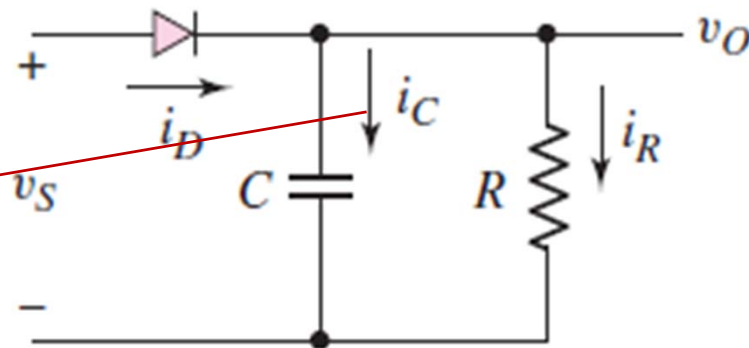

$$i_D = i_C + i_R = C \frac{dv_O}{dt} + \frac{v_O}{R}$$

$$v_O = V_M \cos \omega t$$

$$v_O = V_M \cos \omega t \cong V_M \left[1 - \frac{1}{2}(\omega t)^2 \right] \rightarrow \text{OK for smaller frequency}$$

$$i_C = C \frac{dv_O}{dt} = C V_M \left[-\frac{1}{2}(2)(\omega t)(\omega) \right] = -\omega C V_M \omega t$$

$$i_{C,\text{peak}} = -\omega C V_M [\omega(-\Delta t)] = +\omega C V_M \omega \Delta t$$

$$V_L = V_M \cos[\omega(-\Delta t)] \cong V_M \left[1 - \frac{1}{2}(\omega \Delta t)^2 \right]$$

$$\omega \Delta t = \sqrt{\frac{2V_r}{V_M}} \quad V_r = V_M - V_L$$

$$V_r = \frac{V_M}{2fRC} \quad fC = \frac{V_M}{2RV_r} \quad 2\pi fC = \omega C = \frac{\pi V_M}{RV_r}$$

$$i_{C,\text{peak}} = \left(\frac{\pi V_M}{R V_r} \right) V_M \left(\sqrt{\frac{2 V_r}{V_M}} \right)$$

$$i_{C,\text{peak}} = \pi \frac{V_M}{R} \sqrt{\frac{2 V_M}{V_r}}$$

$$i_{C,\text{avg}} = \frac{\pi}{2} \frac{V_M}{R} \sqrt{\frac{2 V_M}{V_r}}$$

As charging current through capacitor is triangular

$$i_L \cong \frac{V_M}{R}$$

Ignoring changing voltage, current through the load during charging time

$$i_{D,\text{peak}} \cong \frac{V_M}{R} \left(1 + \pi \sqrt{\frac{2 V_M}{V_r}} \right)$$

$$i_{D,\text{avg}} \cong \frac{V_M}{R} \left(1 + \frac{\pi}{2} \sqrt{\frac{2 V_M}{V_r}} \right)$$

→ During conduction time

$$i_{D(\text{avg})} = \frac{V_M}{R} \left(1 + \frac{\pi}{2} \sqrt{\frac{2 V_M}{V_r}} \right) \frac{\Delta t}{T}$$

→ During entire signal period

For full wave rectifier:

$$\omega \Delta t = \sqrt{\frac{2V_r}{V_M}} \longrightarrow \Delta t = \frac{1}{\omega} \sqrt{\frac{2V_r}{V_M}} = \frac{1}{2\pi f} \sqrt{\frac{2V_r}{V_M}}$$

$$\frac{\Delta t}{T} = \frac{1}{2\pi f} \sqrt{\frac{2V_r}{V_M}} 2f = \frac{1}{\pi} \sqrt{\frac{2V_r}{V_M}}$$

$$i_D(\text{avg}) = \frac{1}{\pi} \sqrt{\frac{2V_r}{V_M}} \frac{V_M}{R} \left(1 + \frac{\pi}{2} \sqrt{\frac{2V_M}{V_r}} \right)$$