

# **Clipper & Clamper Circuits**


## GOAL:

Nonlinear characteristics of diodes to create waveshaping circuits known as clippers and clampers.
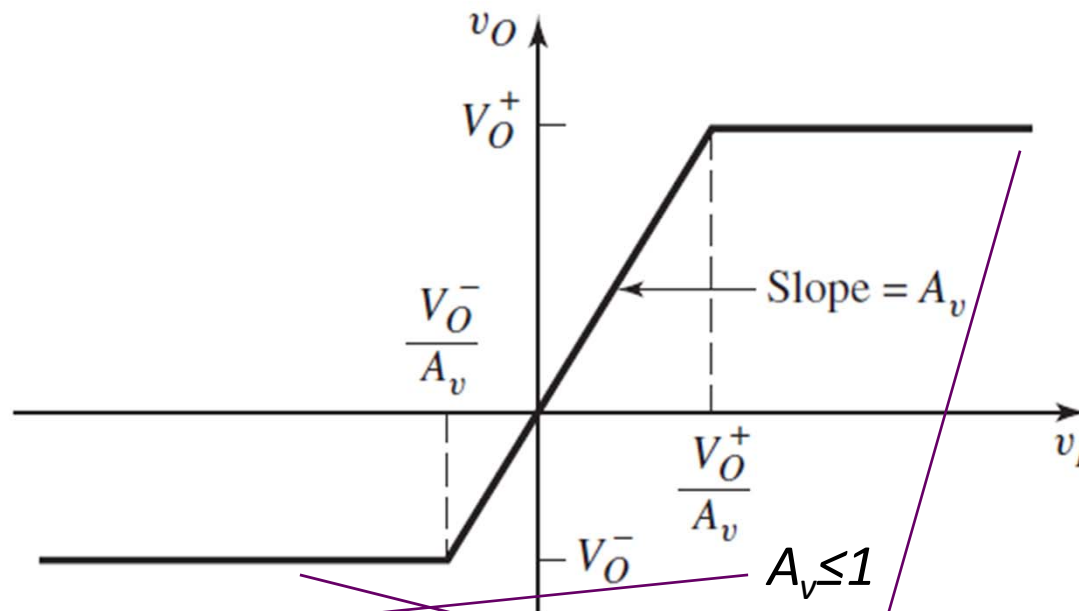
## Clippers:


**Clipper** circuits, also called **limiter** circuits, are used to **eliminate** portions of a signal that are **above** or **below** a specified **level**.

- The **half-wave rectifier** is a **clipper circuit**, since all voltages **below zero** are eliminated.
- An application prevents **breakdown of transistors** in circuits.




A **passive limiter**. A **double limiter**, in which both the positive and negative peak values of the input signal are clipped

## Single diode clipper:

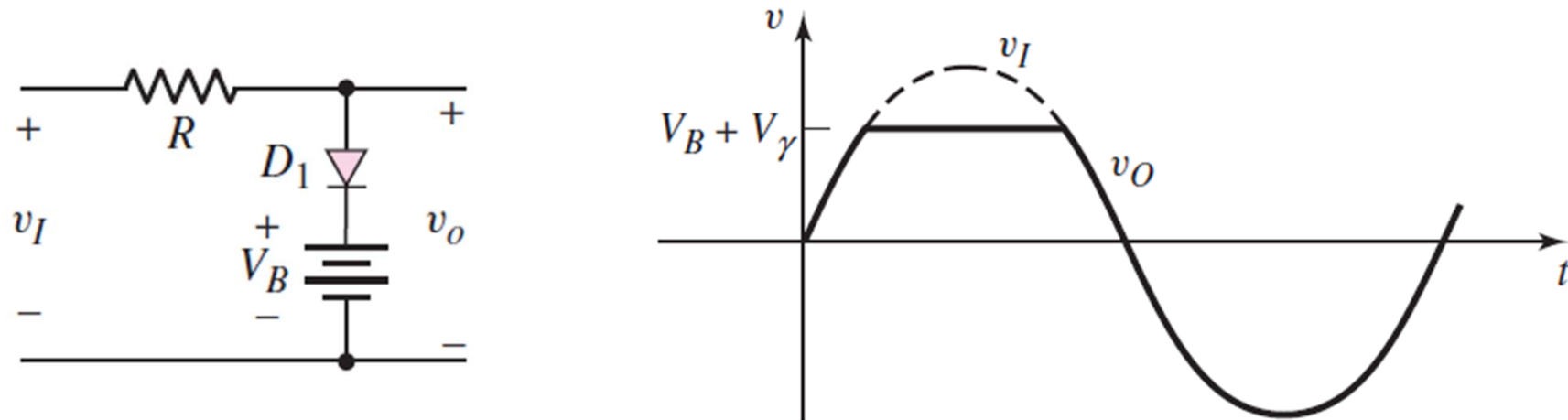


Diode clipper circuits can also be designed such that the **dc power supply** is in **series** with the **input signal**.

If, ideal diode

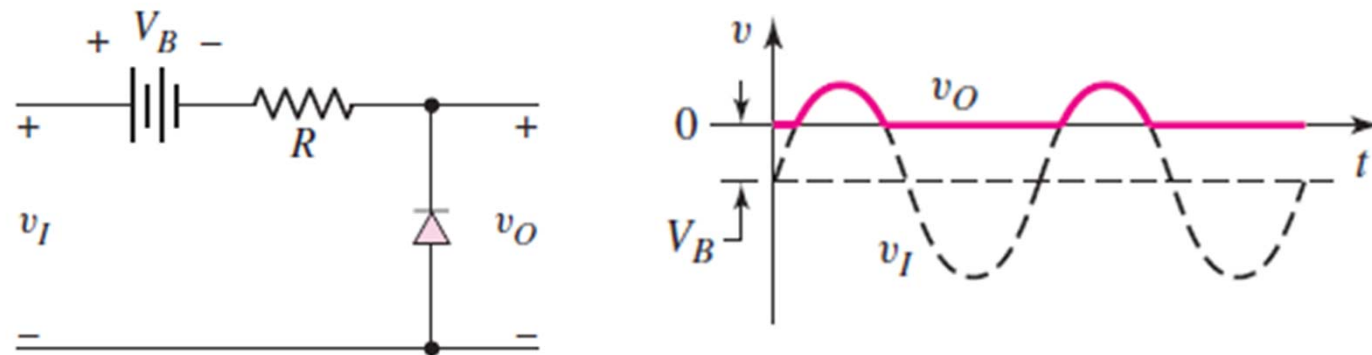




## Multiple diode clipper:

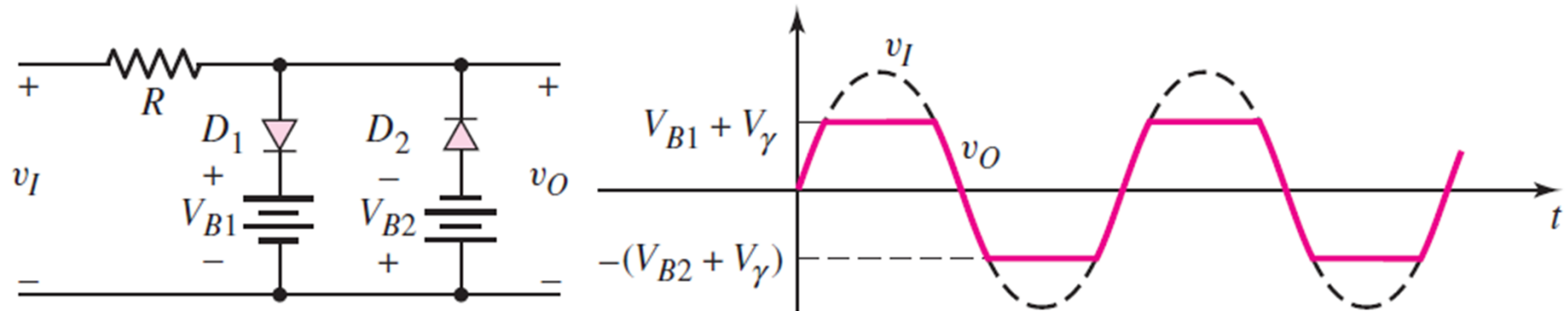

Double limiter or a parallel-based clipper

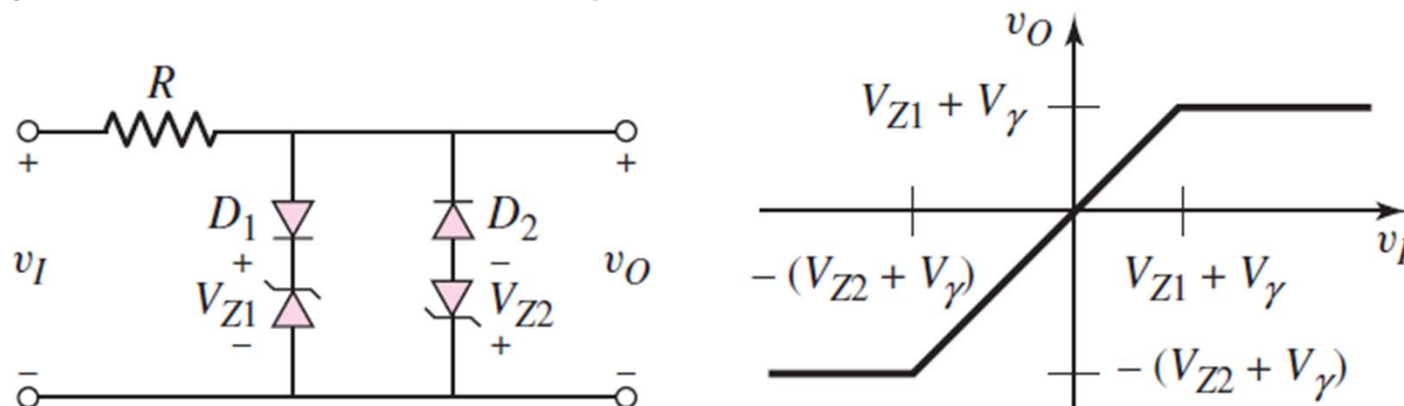**Zener diodes**, operated in the reverse breakdown region, provide essentially **a constant voltage drop**. So, replace **batteries by Zener diodes**.




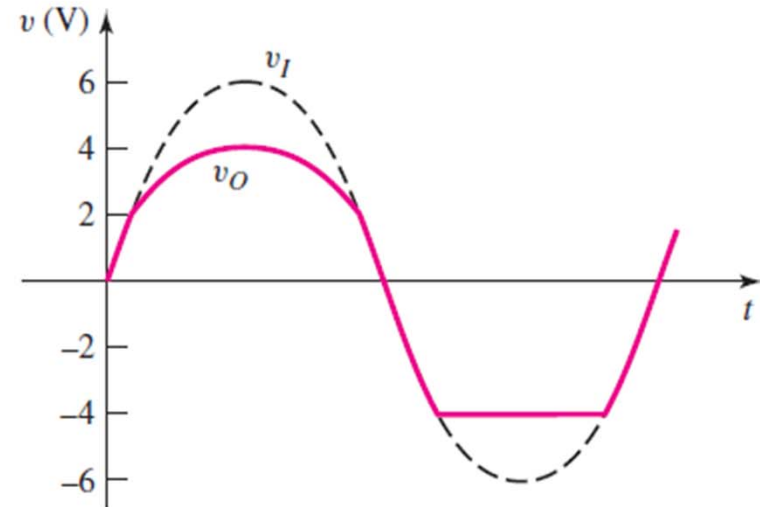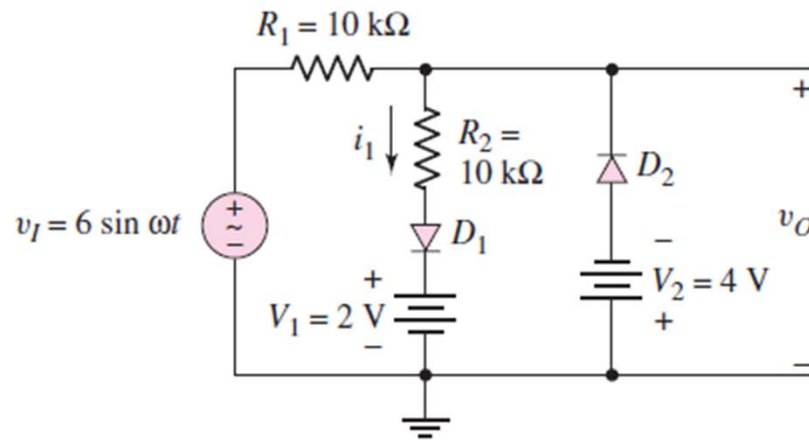

If, ideal diode

$$i_1 = \frac{v_I - 2}{10 + 10}$$
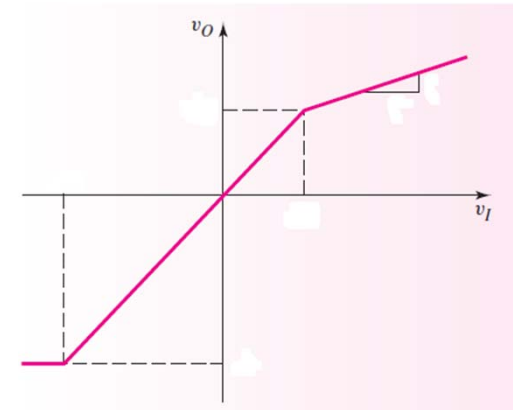
$$v_O = i_1 R_2 + 2 = \frac{1}{2}(v_I - 2) + 2 = \frac{1}{2}v_I + 1$$




Linear relation

## Clampers:


Clamping **shifts** the **entire signal voltage** by a **dc level**.

It adjusts the dc level without needing to know the exact waveform

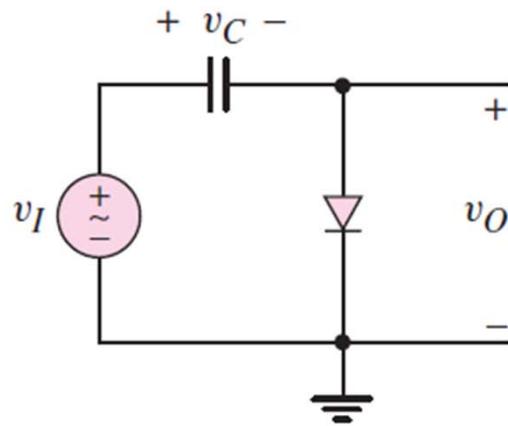Analysis assuming **ideal diode** (diode resistance and cut-in voltage is 0) and **capacitor in steady-state** (does not discharge!)




(a)

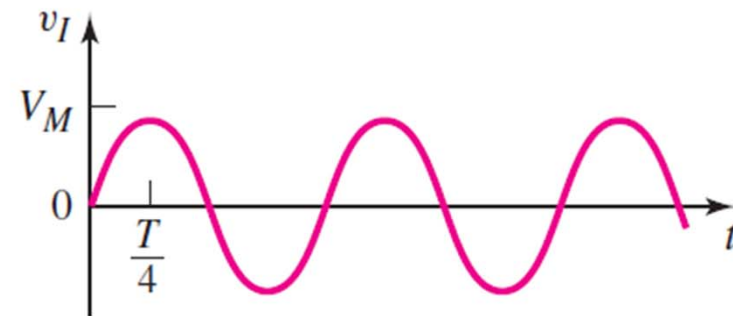

(b)



(c)

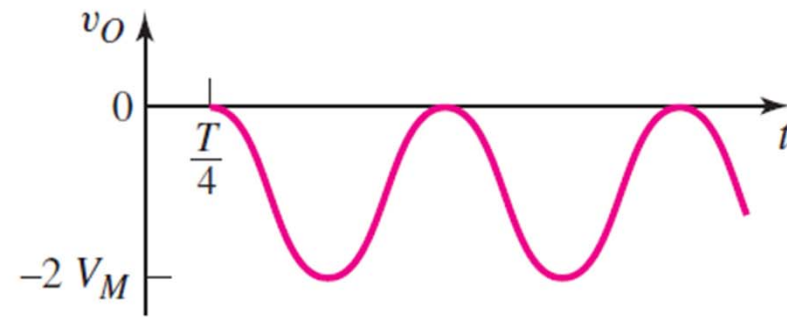


(d)

$$v_O = -v_C + v_I = -V_M + V_M \sin \omega t$$

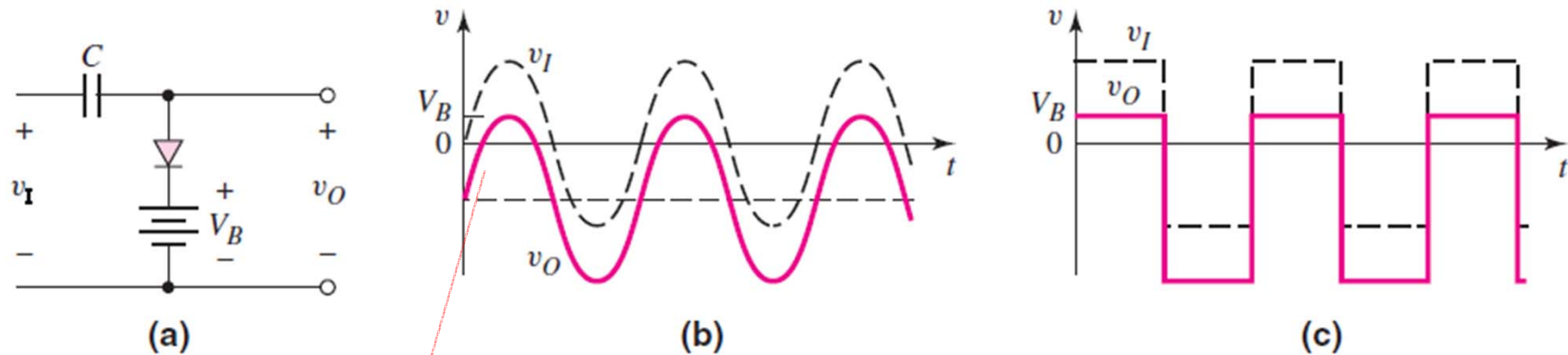Output voltage is “clamped” at zero volts.







**$R_L C \rightarrow$  very large (so that uncharged capacitor does not charge when diode is reversed biased)**

$$v_o = v_I, \text{ diode r. bias}$$

$$v_o = V_B, \text{ diode f. bias}$$

$$v_o = v_I - V_C = v_I - (V_M - V_B)$$

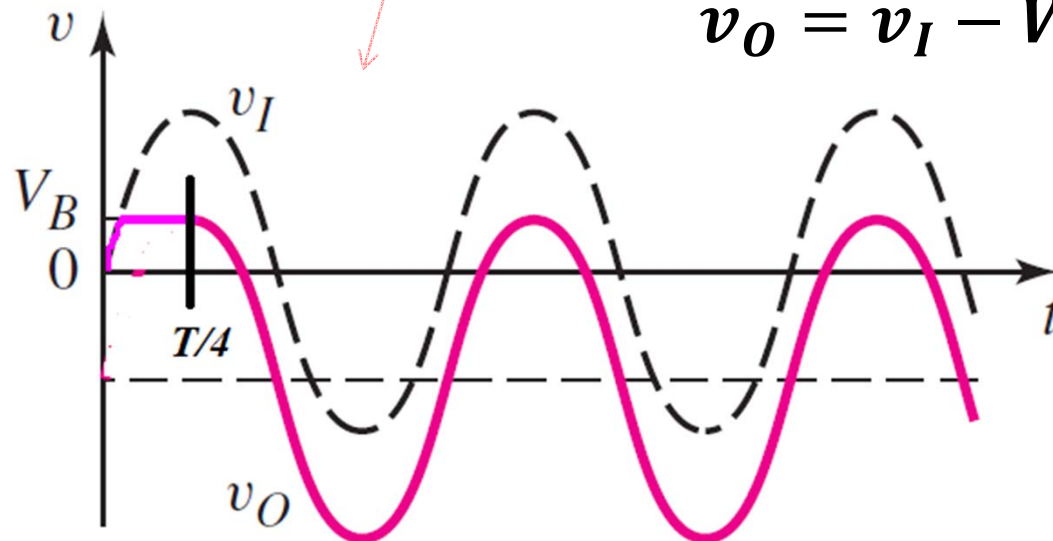

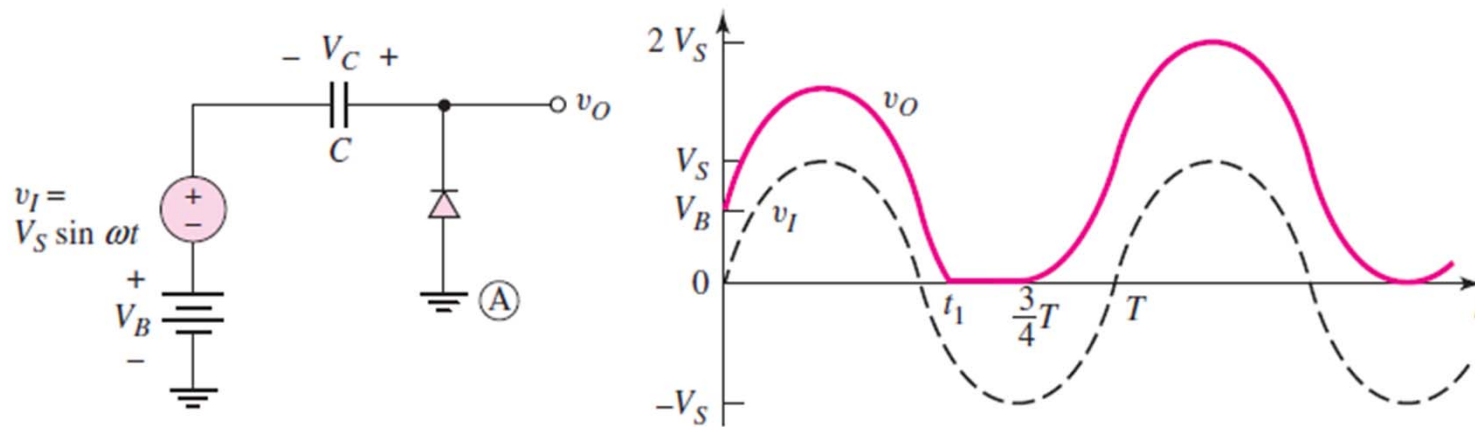

$$v_I + V_B \geq 0$$

$R_L C \rightarrow \infty$  Capacitor does not charge


**Output:**  $v_O = v_I + V_B$

$$v_I + V_B < 0 \quad \text{Output: } v_O = 0 \quad V_C = V_S - V_B$$


$$v_I > -V_S + V_B$$


**Output:**  $v_O = v_I + V_B + V_C = v_I + V_S$

# **Multiple-Diode Circuits**

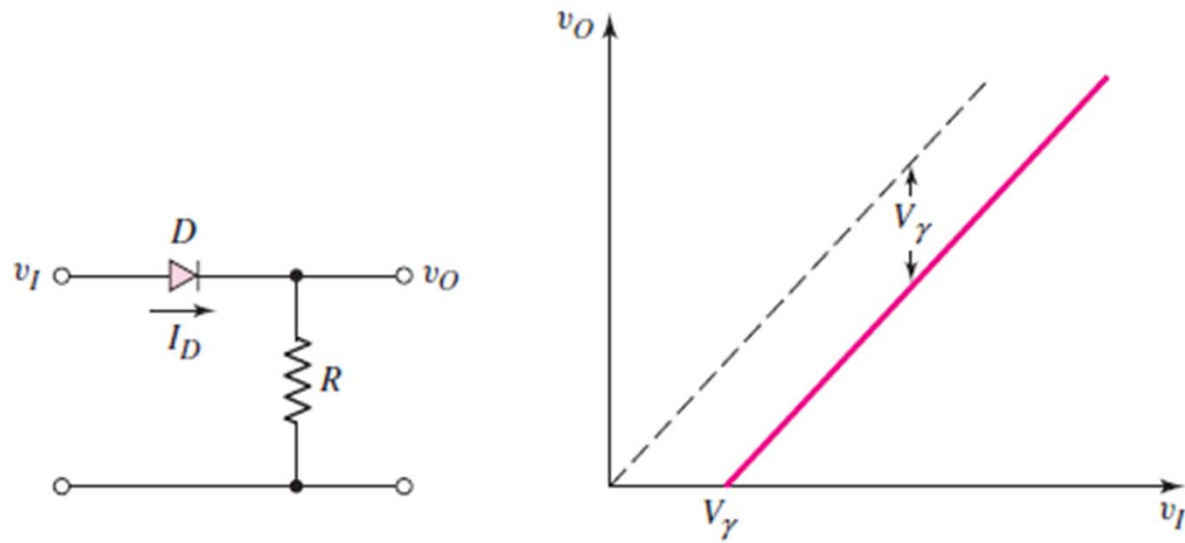

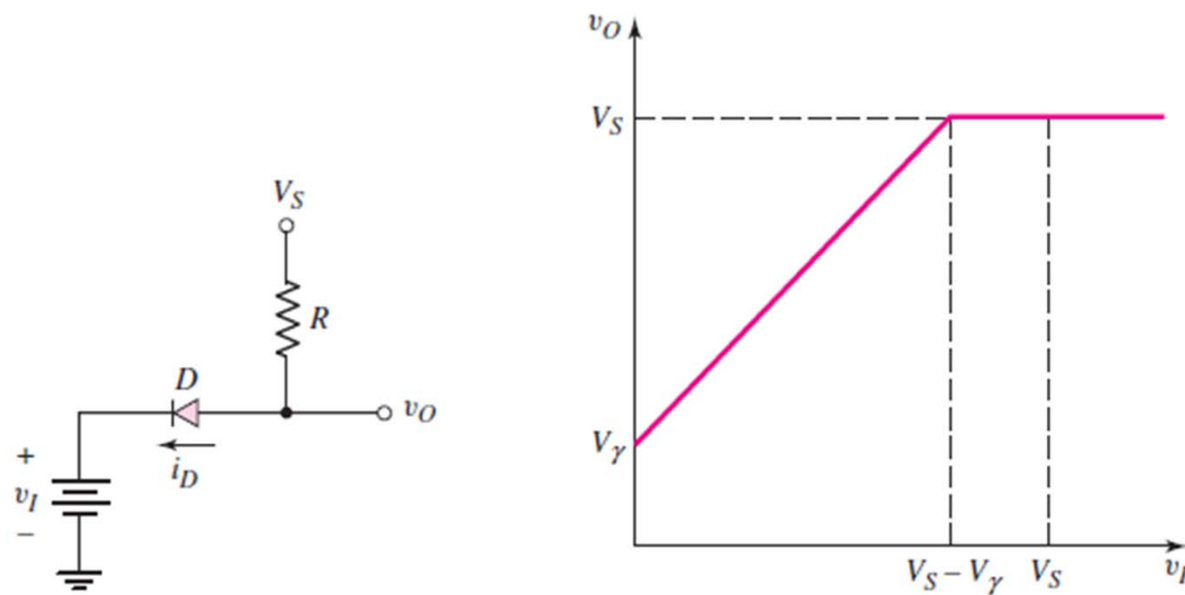Piecewise linear nature of the diode and the diode circuit



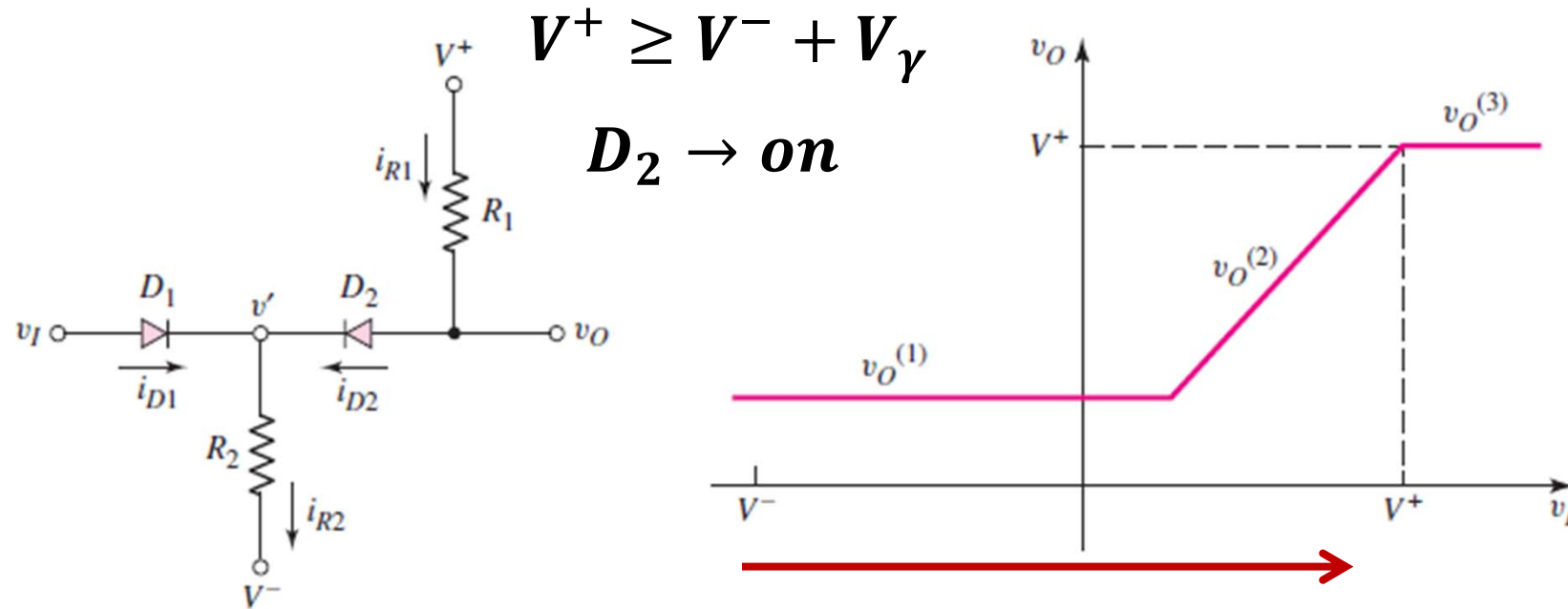


$v_I = V^-: D_1 \rightarrow off, \text{ as } v' \geq V^-$

$$V^+ - \textcolor{red}{v_O} = \textcolor{blue}{i_{R1}} R_1$$

$$V^+ - V_\gamma - V^- = (R_1 + R_2) \textcolor{blue}{i_{R1}}, i_{R1} = i_{R2} = i_D$$

$$v' = v_O - V_\gamma, \quad v_I < v' + V_\gamma = v_O: D_1 \rightarrow off$$
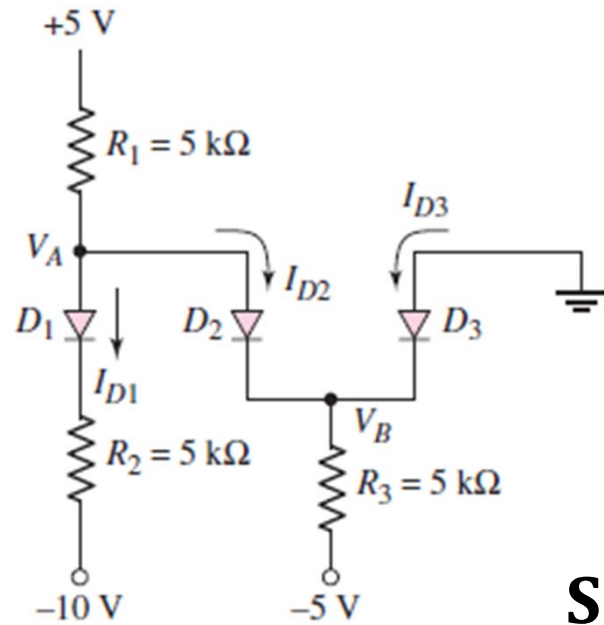
$$v_I = \textcolor{red}{v_O}: D_1 \rightarrow on \text{ till } v_I < V^+. \quad v_I \geq V^+, \textcolor{red}{v_O} = V^+$$



**Assume  $D_1, D_2$  &  $D_3$  conducting**

$$V_A, V_B, I_{R1}, I_{D1} \rightarrow I_{D2} = -ive$$

**So assume only  $D_1$  &  $D_3$  conducting**


**Leads to  $I_{D1} = +ive$  &  $I_{D3} = +ive$  &  $I_{D2} = 0$**

**Tutorial**

They key is to judiciously guess the initial diodes' states for a given circuit (considering least input) & check whether the guess was right or wrong!

## Diode Logic Circuits:

OR gate

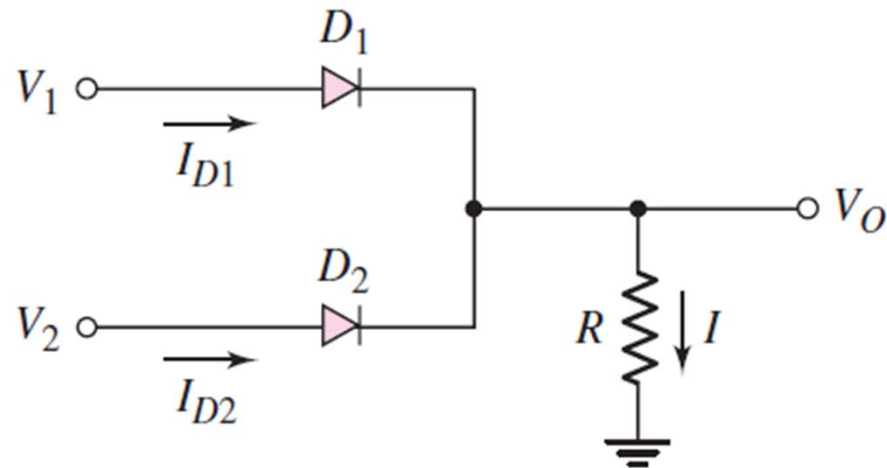


Two-diode OR logic circuit response

$V_1$ (V)	$V_2$ (V)	$V_o$ (V)
0	0	0
5	0	4.3
0	5	4.3
5	5	4.3

Voltages in parallel equals that one voltage whose associated serial resistance is the smallest

## AND gate

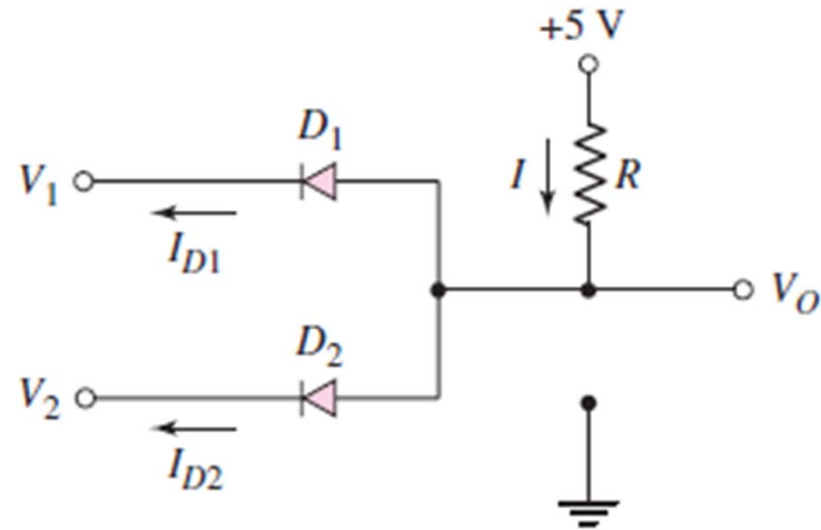

Two-diode AND logic  
circuit response


$V_1$ (V)	$V_2$ (V)	$V_o$ (V)
0	0	0.7
5	0	0.7
0	5	0.7
5	5	5



# **Photodiode & LED Circuits**

## Photodiode circuit:

Reverse bias condition

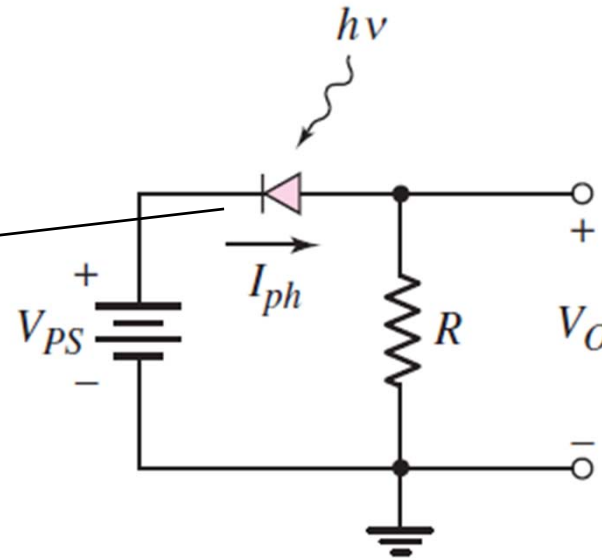

- Photons striking the diode create excess electrons and holes in the space-charge region
- Electric field quickly sweeps carriers out of the space-charge region, thus creating a photocurrent in the reverse-bias direction.

$$I_{ph} = \eta e \Phi A$$

Quantum efficiency

Electronic charge


Photon flux density

Junction area


**Linear relationship** between photocurrent and photon flux is based on the assumption that the **reverse-bias voltage** across the diode is **constant**

**LED circuit:**

Common-anode display

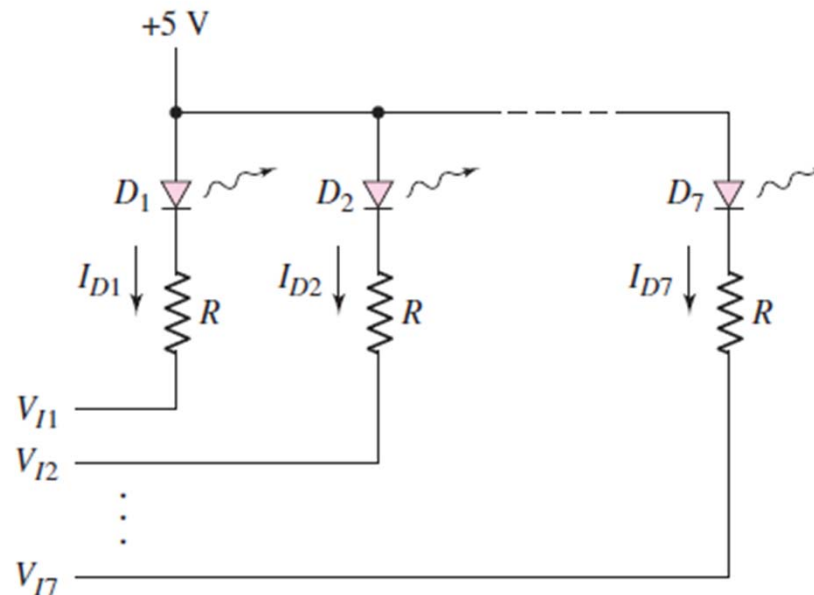
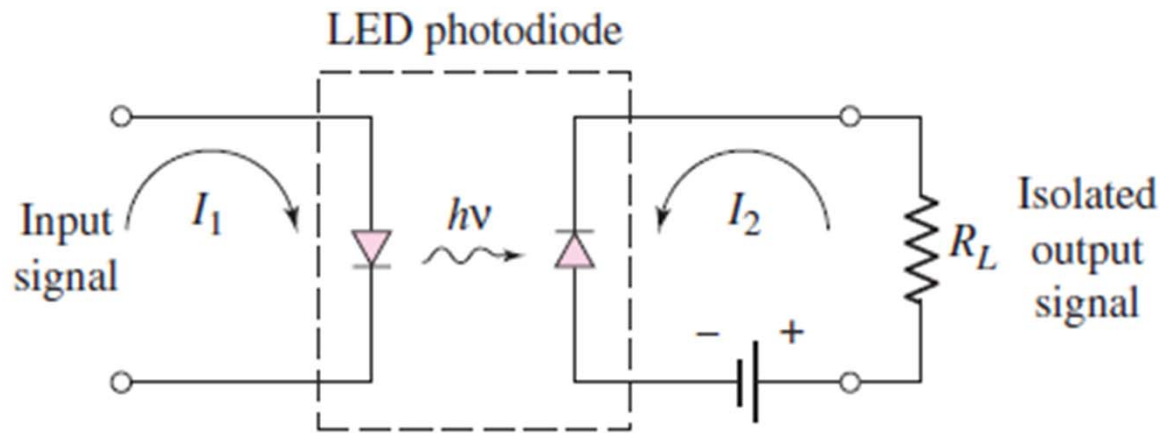
## Application of Photodiode & LED put together



- Opto-isolators, in which the input signal is **electrically decoupled** from the output
- Opto-isolators **prevent high voltages** from affecting the system receiving the signal